

Practical case: Safe Hydraulic Press Control




Safe Hydraulic Press Control

Master Digital Electronics by building a two-hand safety circuit using an AND gate. Ensure the LED load activates only when two inputs trigger simultaneously.

Practical case: Double Key Security System

Double Key Security System

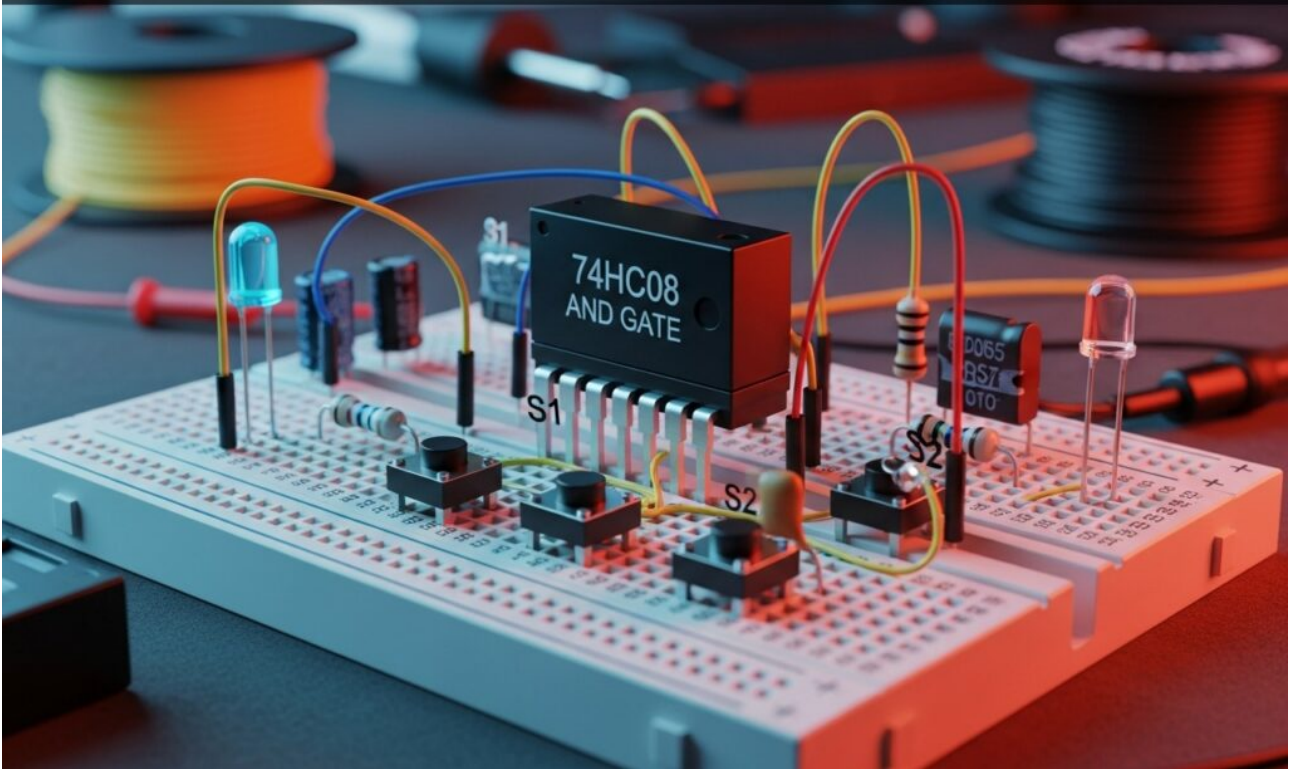

Master Digital Electronics by building a dual-key security alarm with an AND gate. Learn to control logic signals and activate an LED only when inputs match.