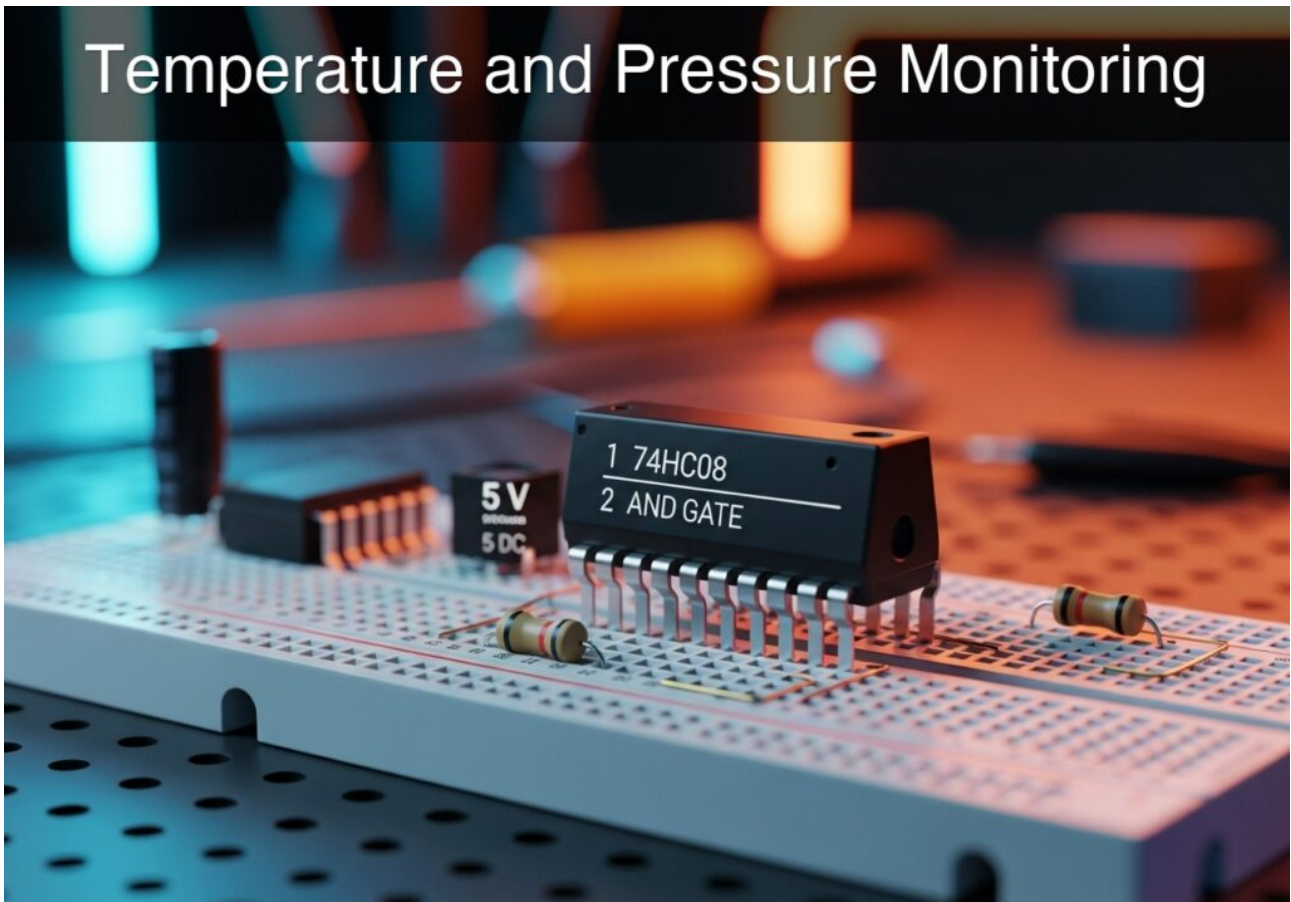


## Practical case: Temperature and Pressure Monitoring




Master Digital Electronics by building an industrial safety circuit. Use an AND gate to trigger an alarm only when both temperature and pressure sensors spike.

---

## Practical case: Vehicle access control with barrier

# Vehicle access control with barrier

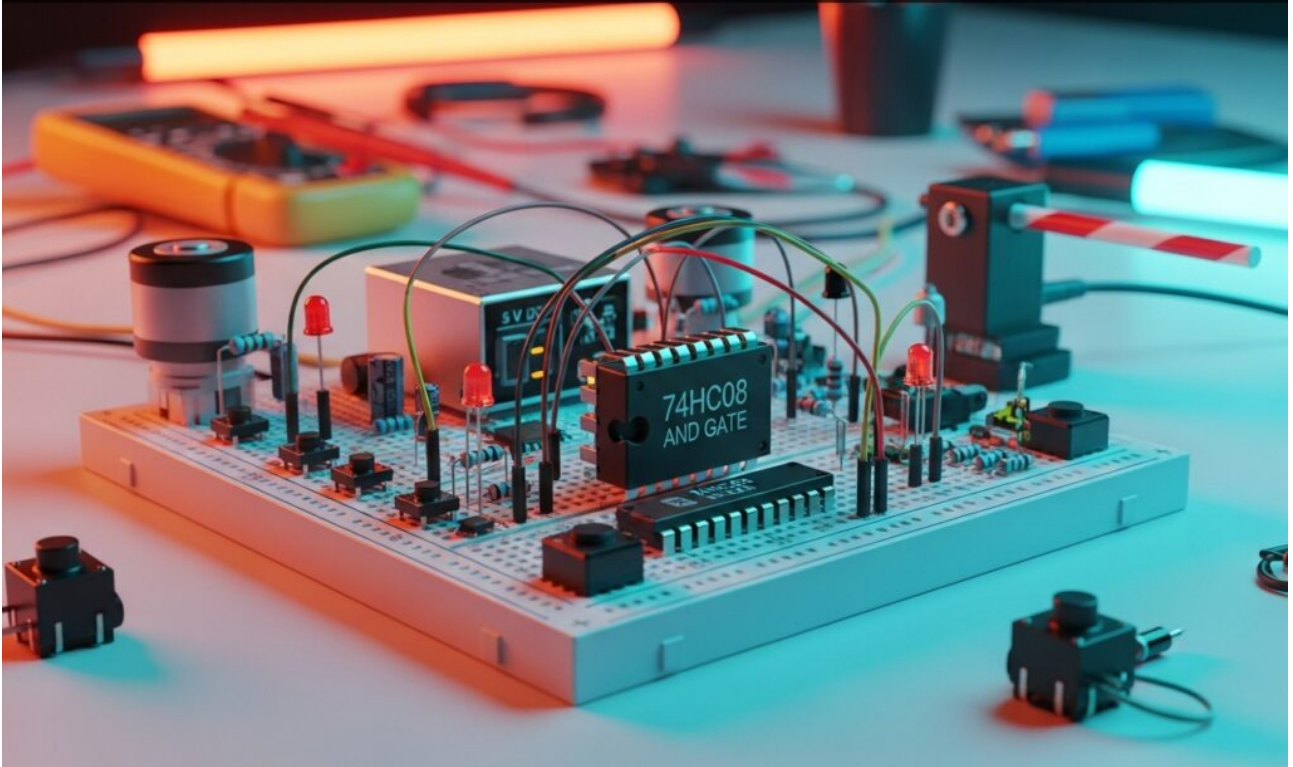

Master Digital Electronics by building a safety barrier circuit. Use a 74HC08 AND gate to trigger a 5V LED signal only when dual inputs activate simultaneously.