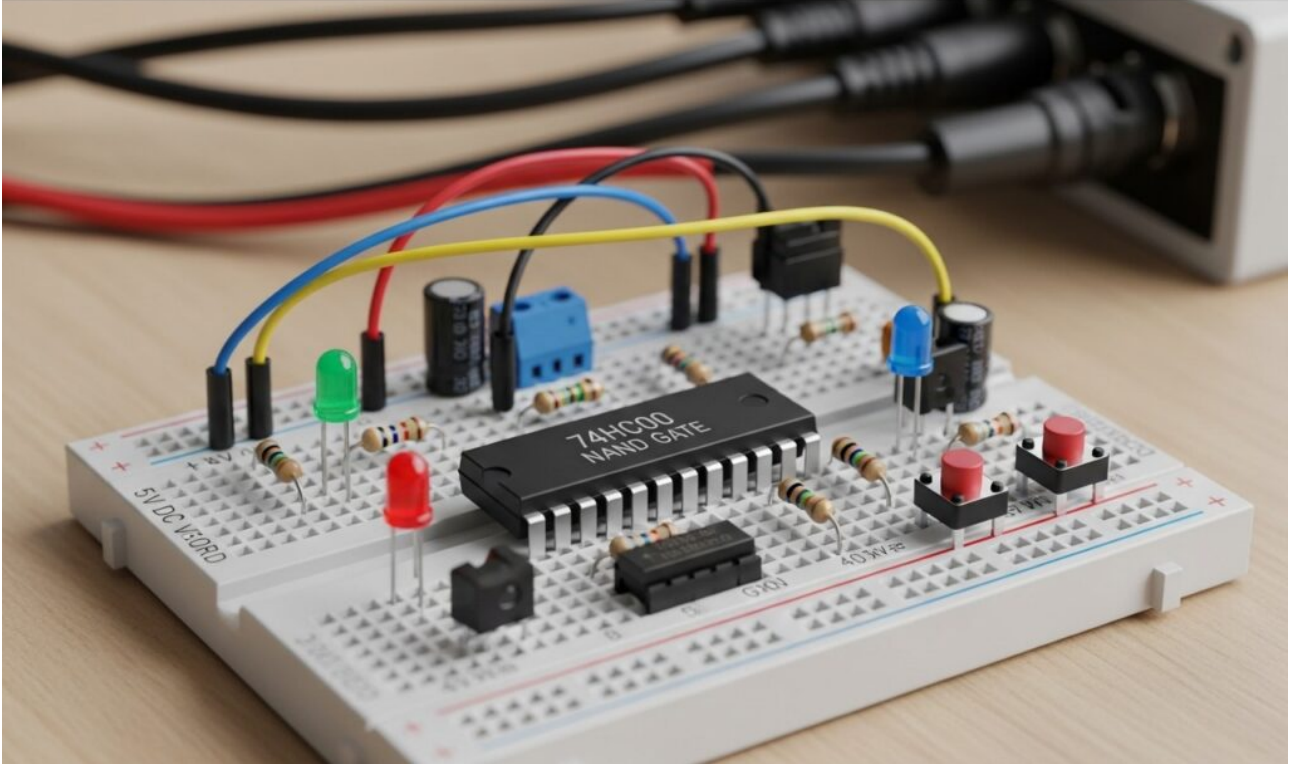


## Practical case: Dual Safety Motor Activation

# Dual Safety Motor Activation




Learn Digital Electronics by building a safety circuit with a NAND gate. Create a two-hand motor control system that activates 5V output only on dual press.

---

## Practical case: Veto Voting System

# Veto Voting System

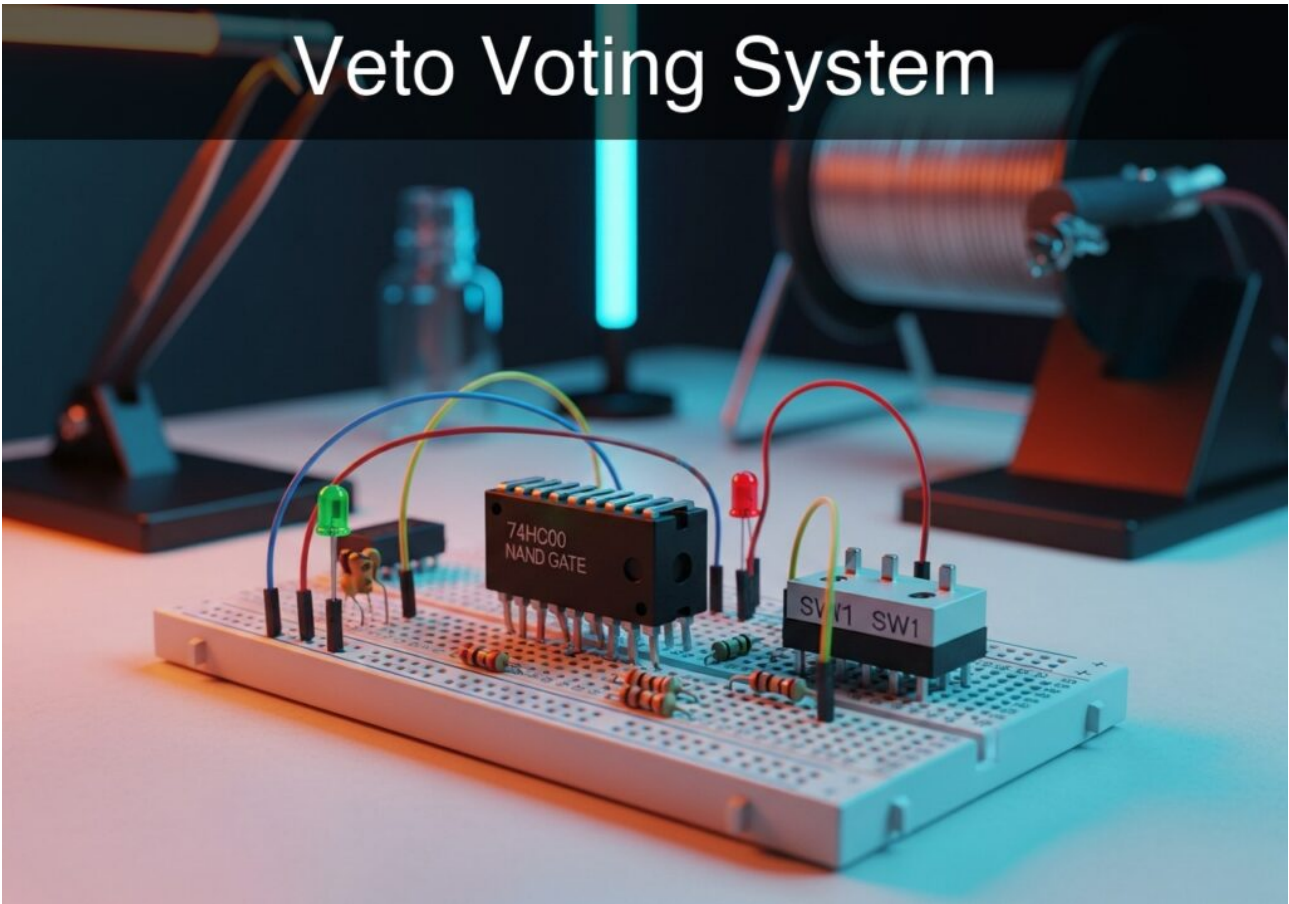


Master Digital Electronics by building a voting system using a single 74HC00 NAND gate IC. Create a safety interlock circuit where LED output signals approval.

---

## Practical case: Water tank level control

# Water tank level control

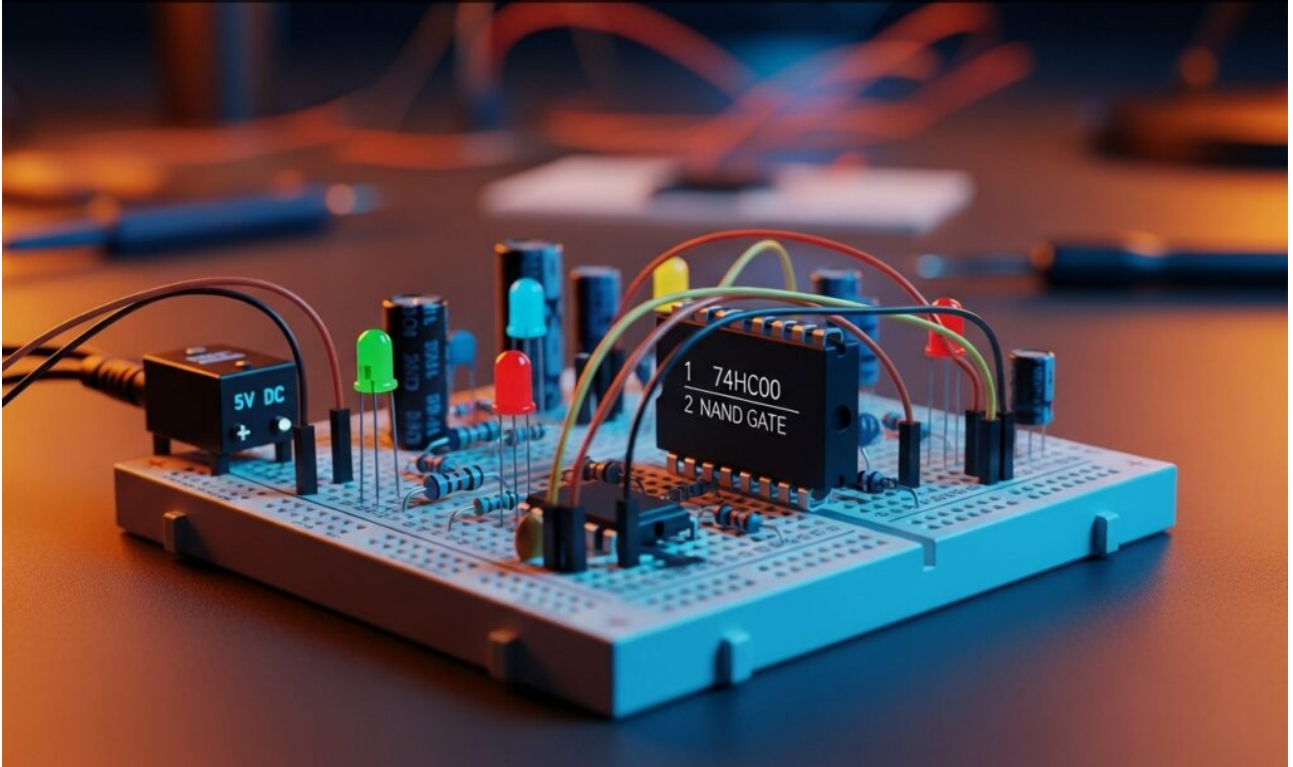


Learn Digital Electronics by building a pump safety stop using a NAND gate. Design a circuit that cuts power to 0V only when two sensors detect a full tank.

---

## **Practical case: Window sensor security alarm**

# Window sensor security alarm

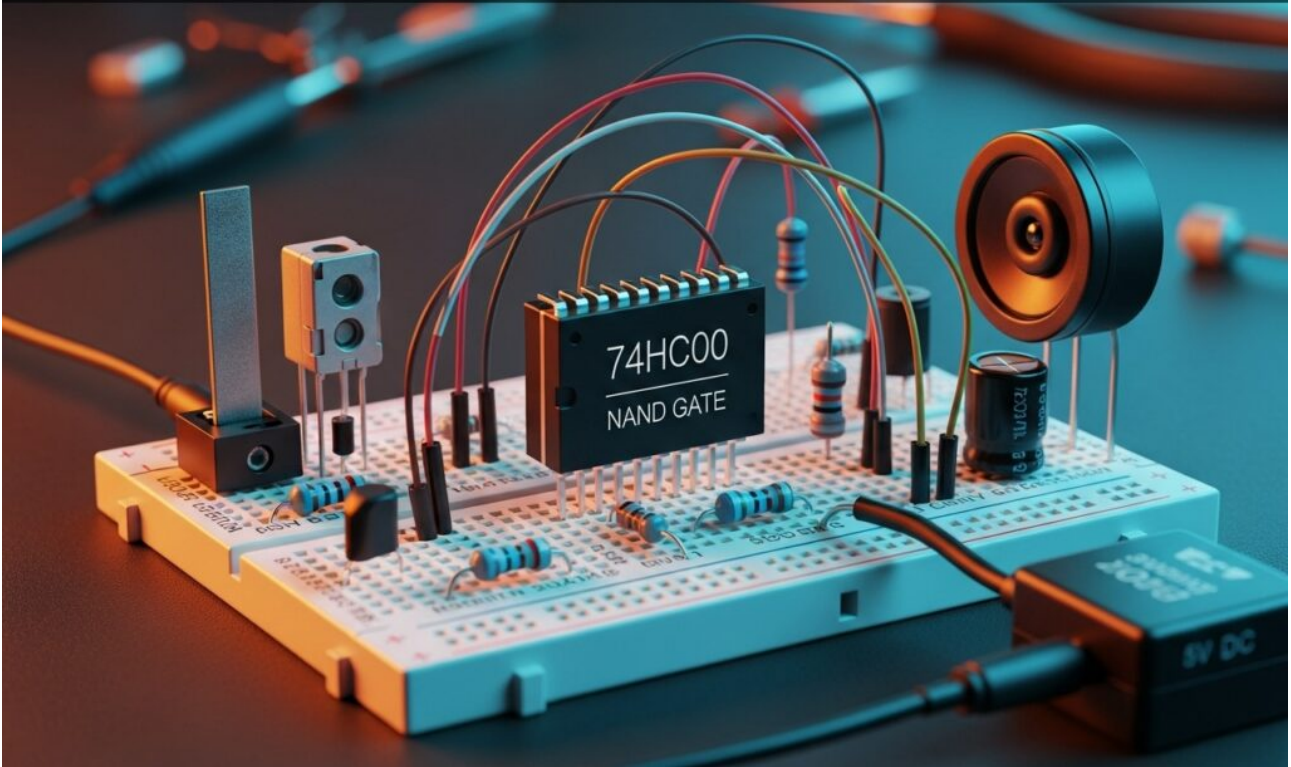


Master Digital Electronics by building a fail-safe alarm with a NAND gate. Detect open windows and trigger a 5V LED signal instantly when security is breached.

---

## Practical case: Empty Tank Level Indicator

# Empty Tank Level Indicator

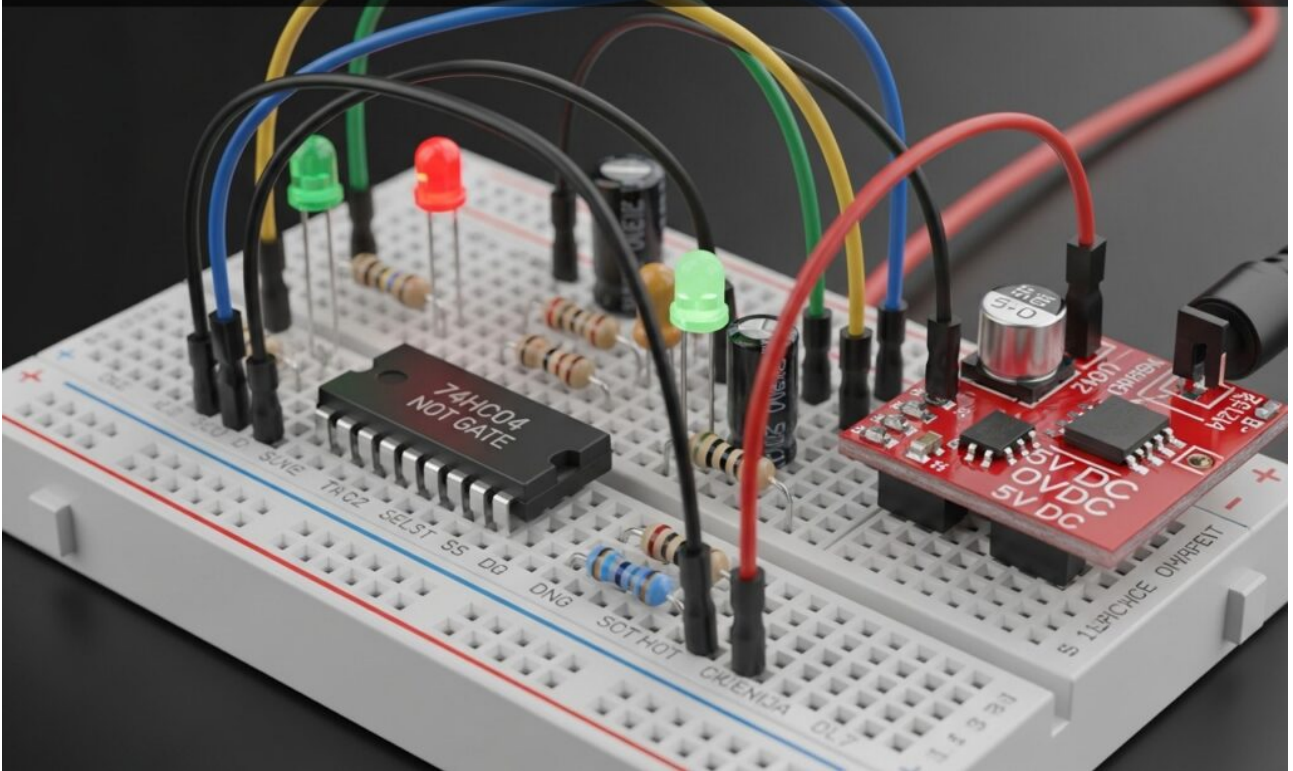


Master Digital Electronics by building a water level alarm with a NOT gate. Design a circuit that lights an LED when tanks empty, preventing pump damage.

---

**Practical case: Emergency deactivation**

# Emergency deactivation

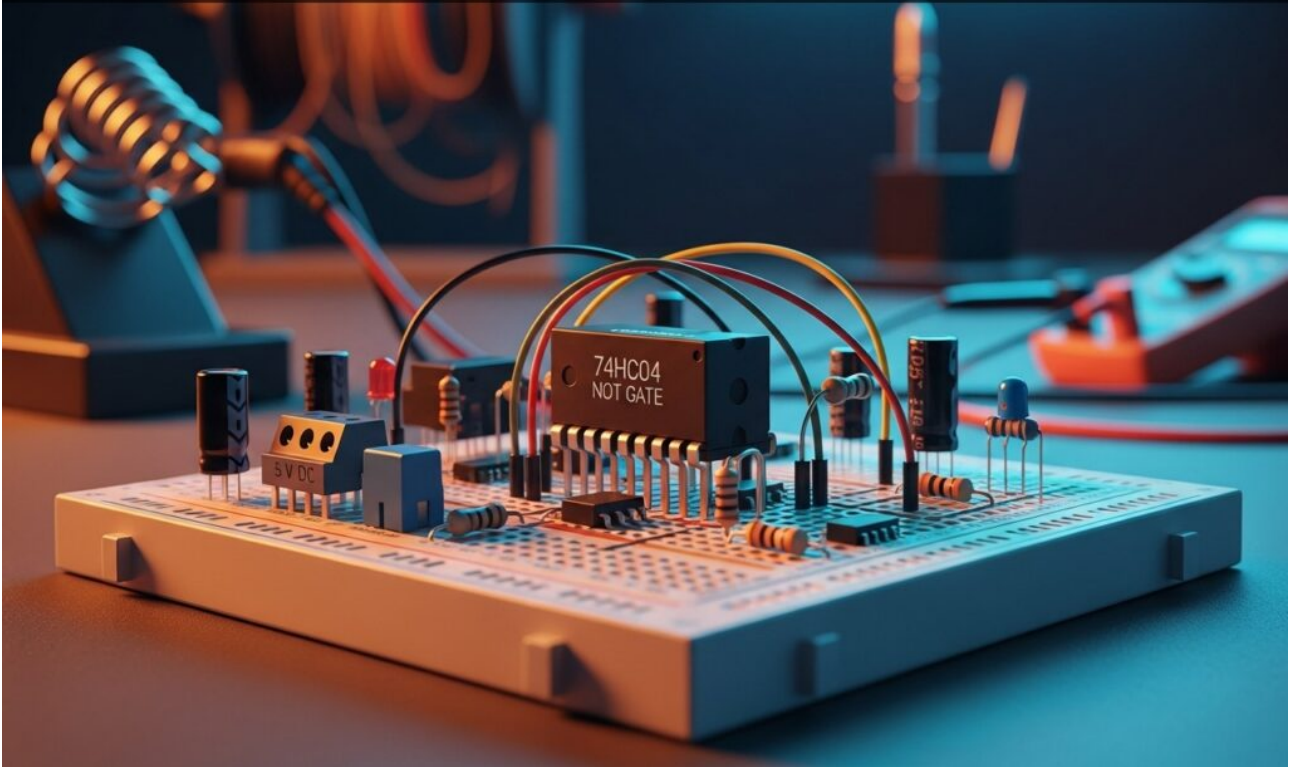

Learn Digital Electronics by building a safety kill switch using a NOT gate. Create a circuit where pressing a button instantly cuts the Ready signal voltage.