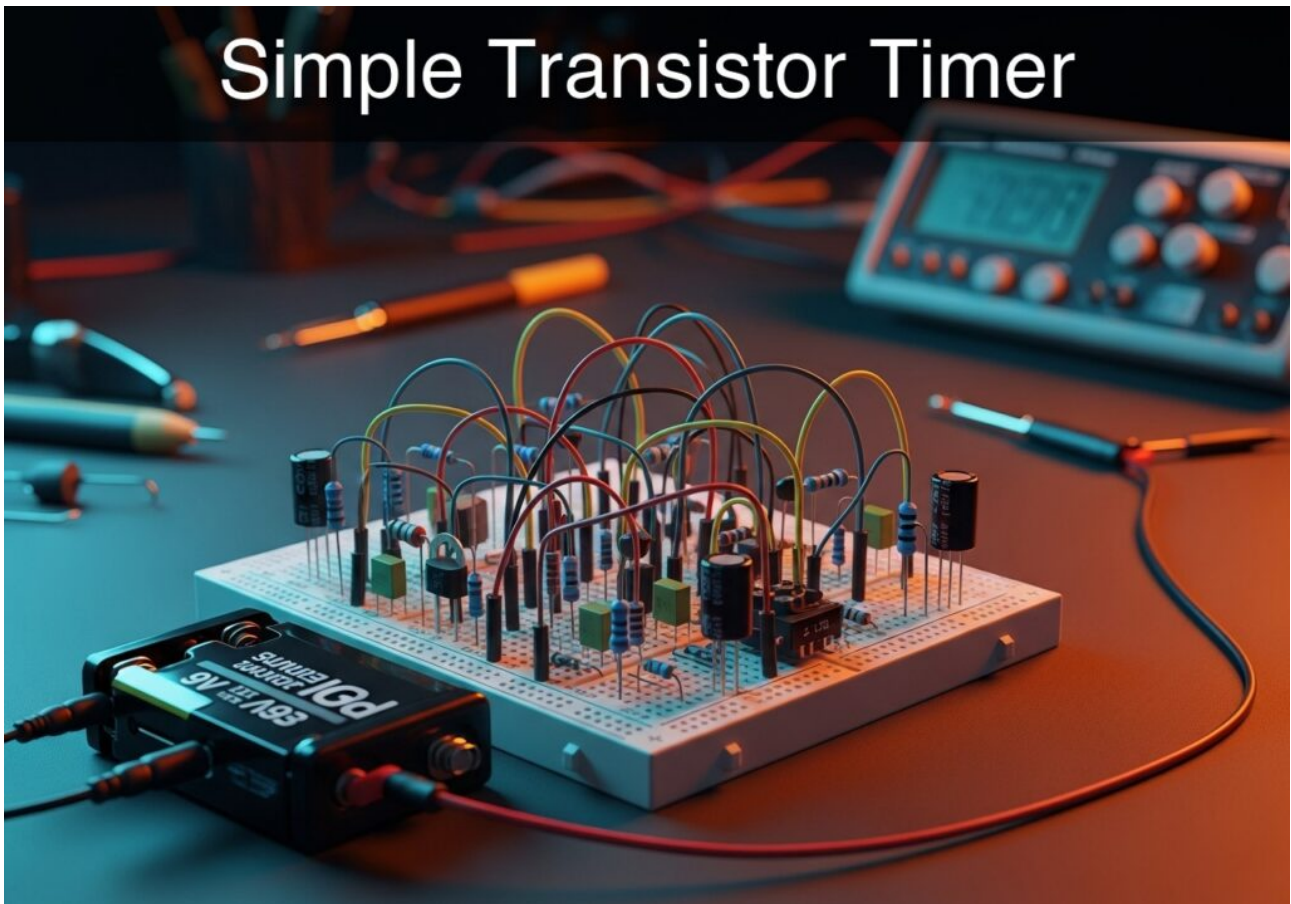


## Practical case: Simple Transistor Timer




Learn Analog Electronics by building a practical off-delay timer. Use a Capacitor to control transistor switching and create custom lighting fade-out effects.

---

## Practical case: DC blocking

# DC blocking

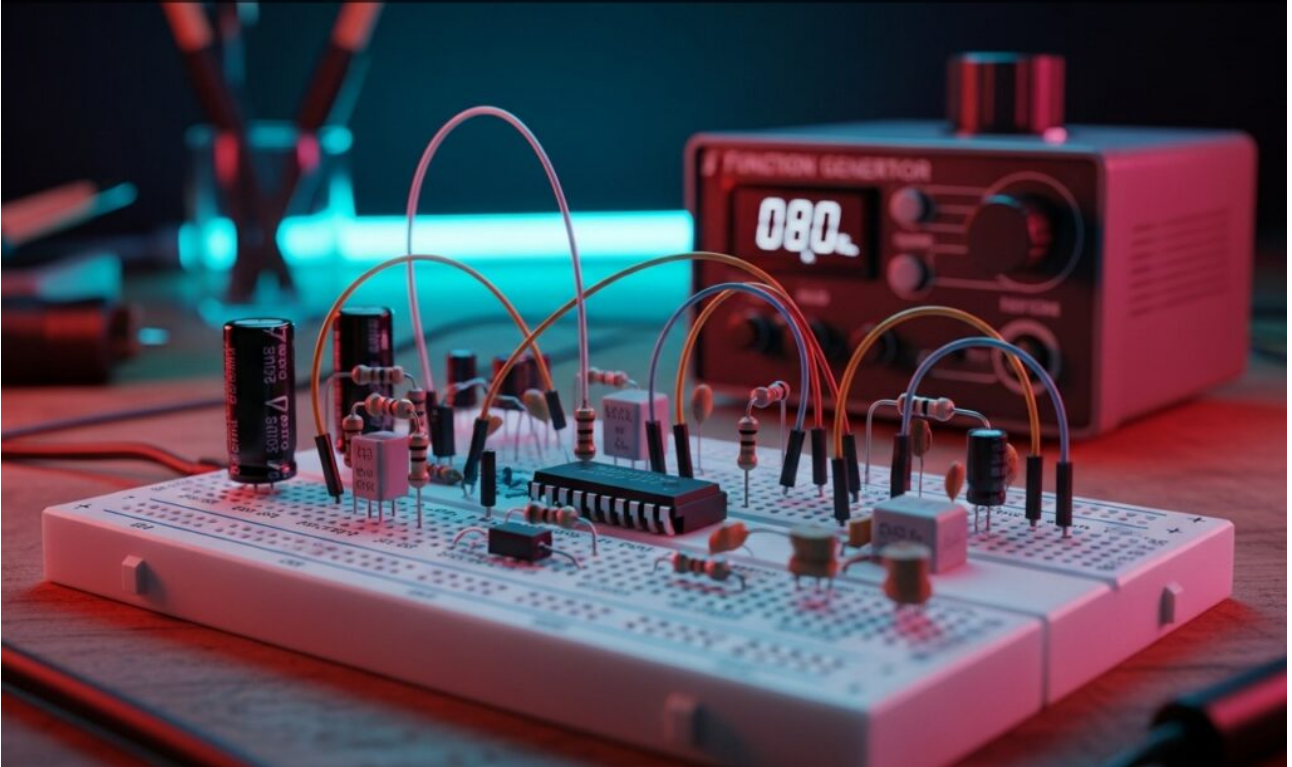


Master Analog Electronics by building a coupling circuit with a Capacitor. Learn to block DC offsets while passing AC audio signals for clear, centered output.

---

## **Practical case: Basic rectifier filtering**

# Basic rectifier filtering

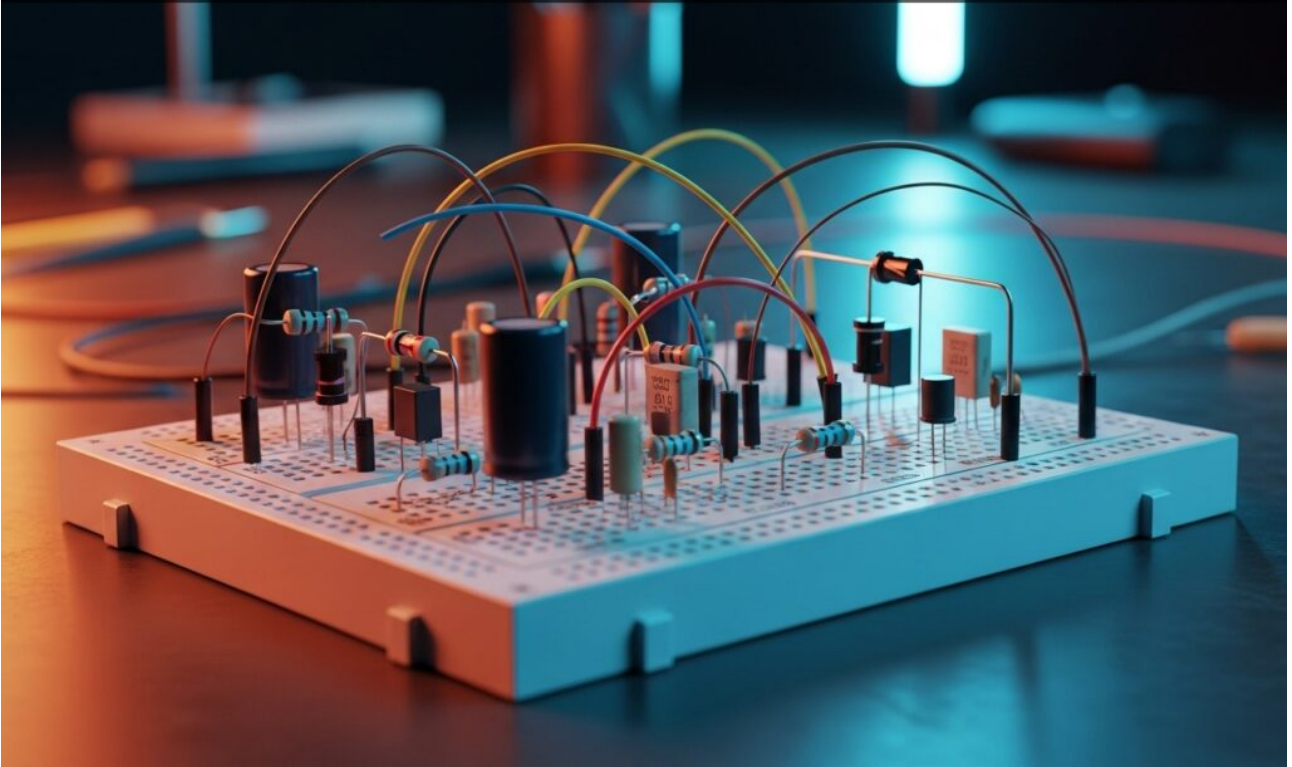


Master Analog Electronics by building a rectifier circuit. See how a Capacitor transforms AC ripple into steady DC voltage for reliable power supplies.

---

**Practical case: Visual Charge and Discharge with LED**

# Visual Charge and Discharge with LED

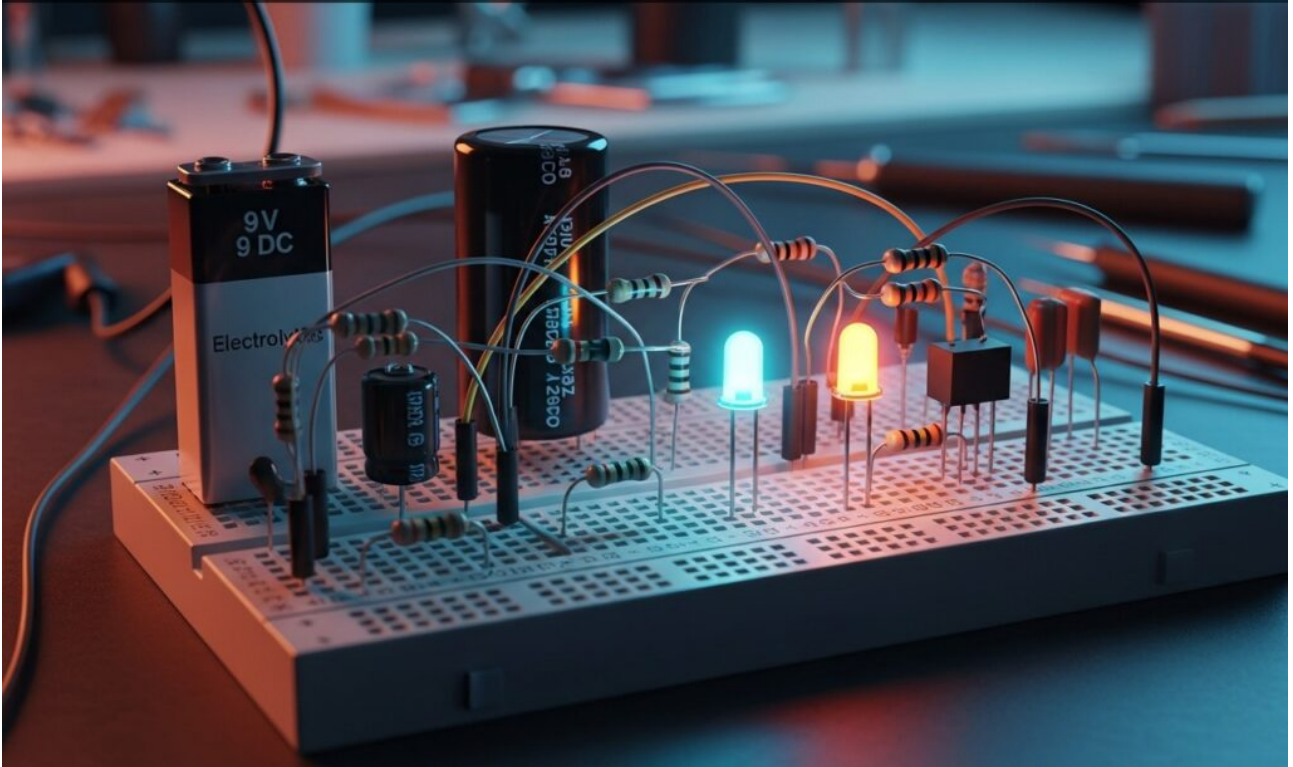

Explore Analog Electronics by building a circuit where a Capacitor keeps an LED fading out after power loss, visualizing energy storage and RC time constants.