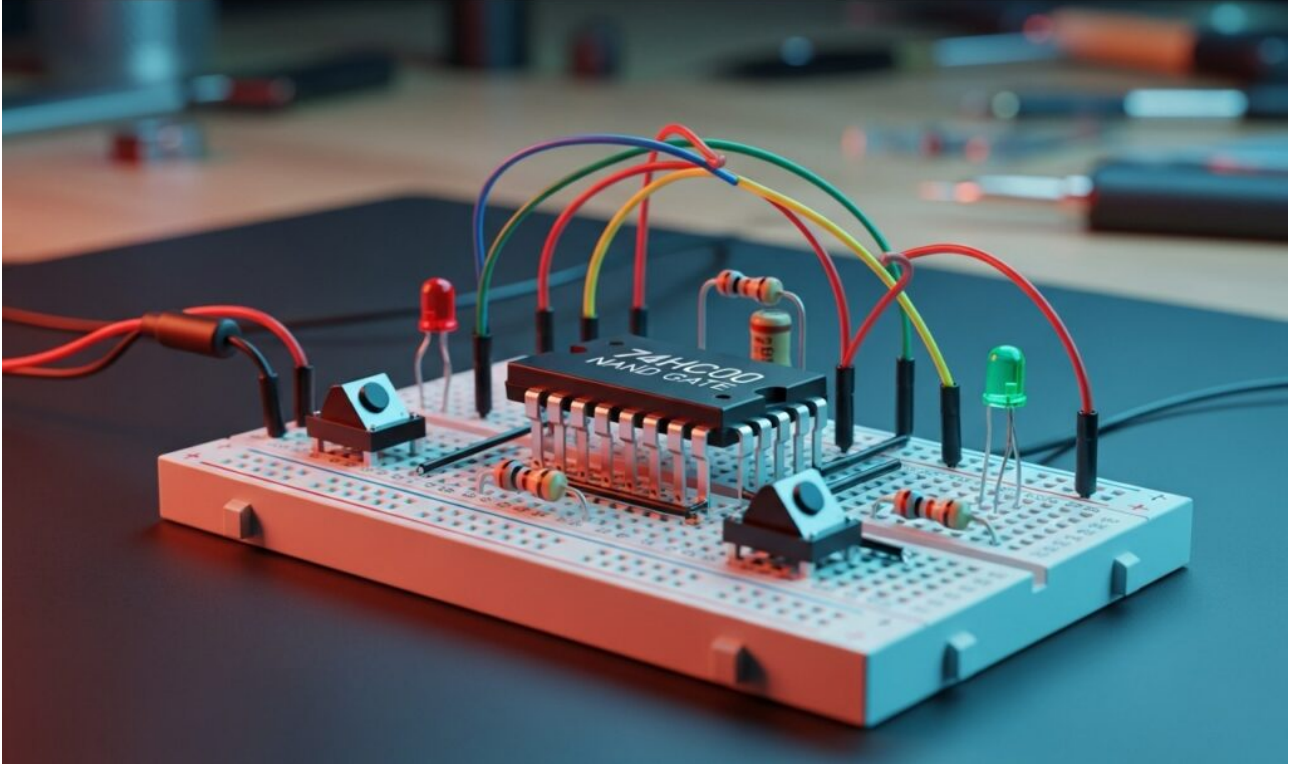


## Practical case: Light switching from two points

# Light switching from two points




Master Digital Electronics by building a 2-way switch using the universal NAND gate. Synthesize XOR logic to toggle LED states based on dual input signals.

---

## Practical case: Debouncing SR Latch with NAND

# Debouncing SR Latch with NAND

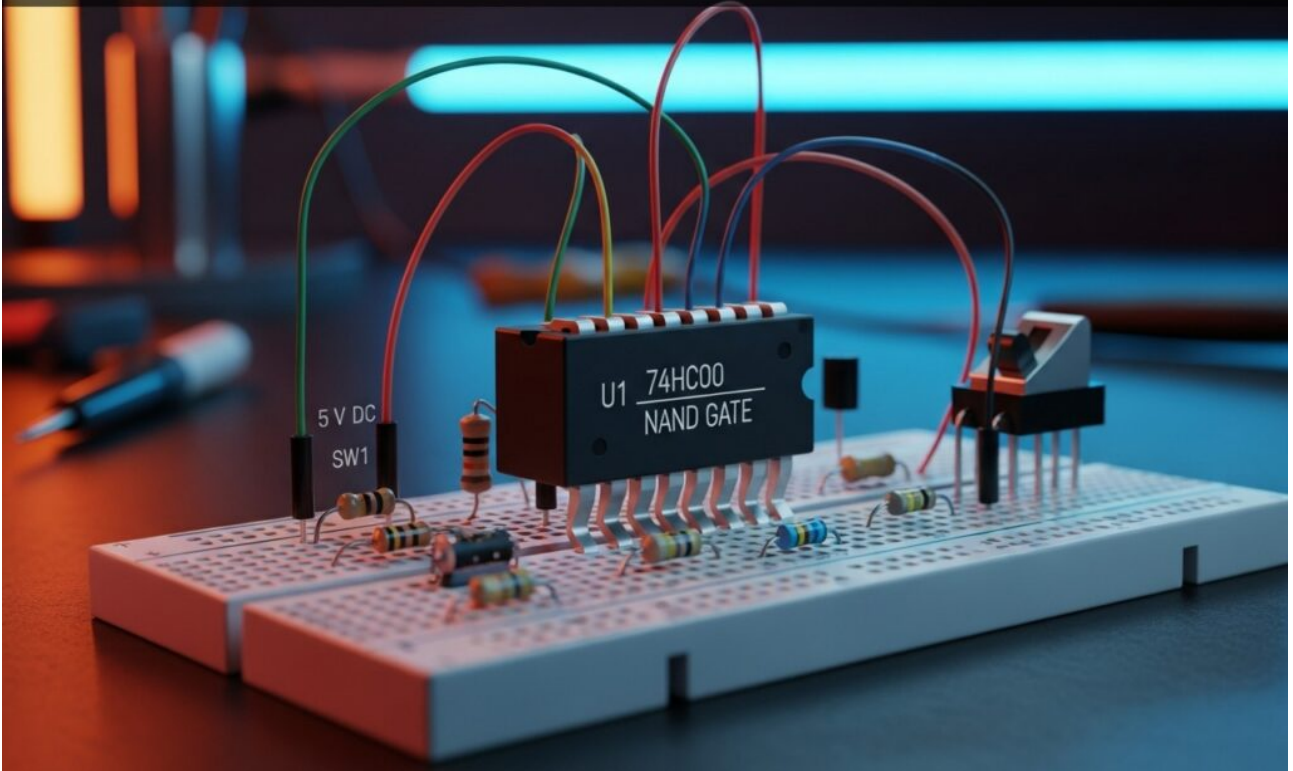

Master Digital Electronics by building a NAND gate SR latch to eliminate switch noise. Ensure clean signals and verify stable memory states with LEDs.