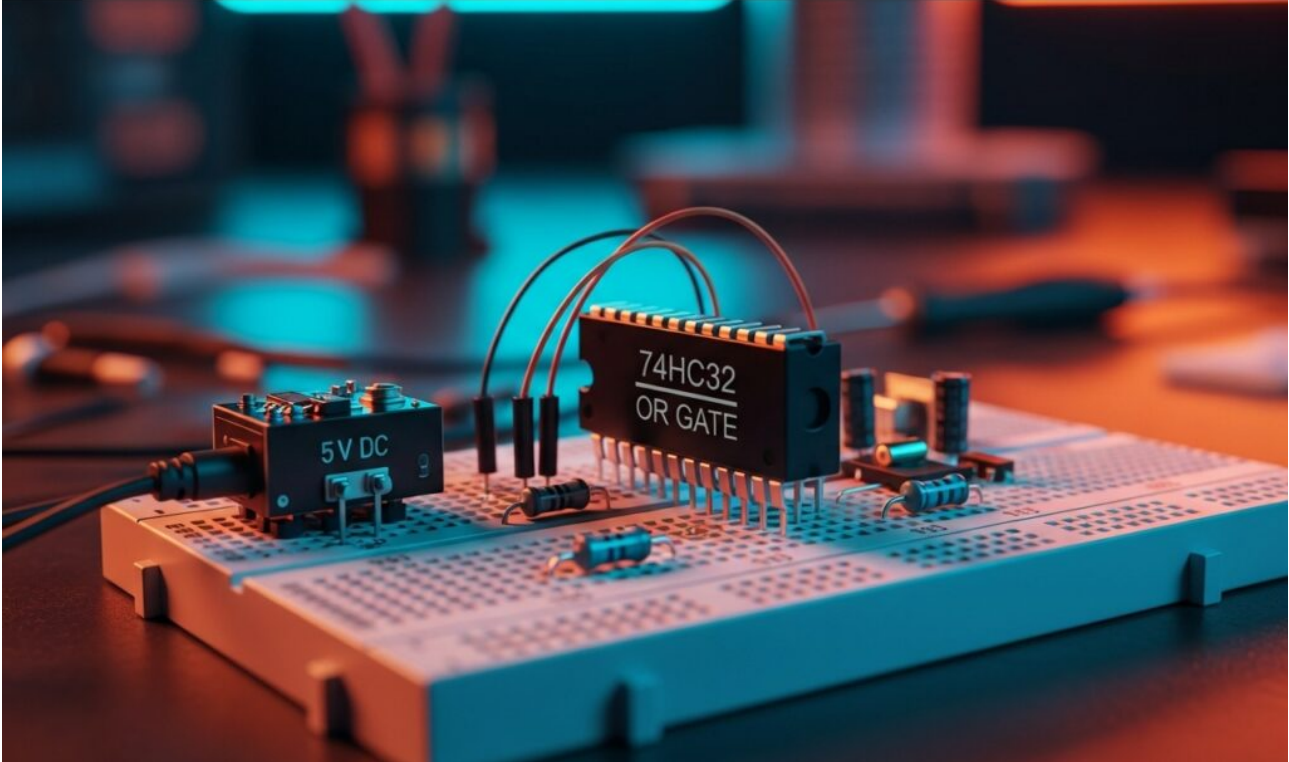


## Practical case: Multi-perimeter intrusion detection

# Multi-perimeter intrusion detection




Master Digital Electronics by building a 4-zone security alarm. Use an OR gate to trigger a relay and siren instantly when any single access point is breached.

---

## Practical case: Simple electronic voting system

# Simple electronic voting system

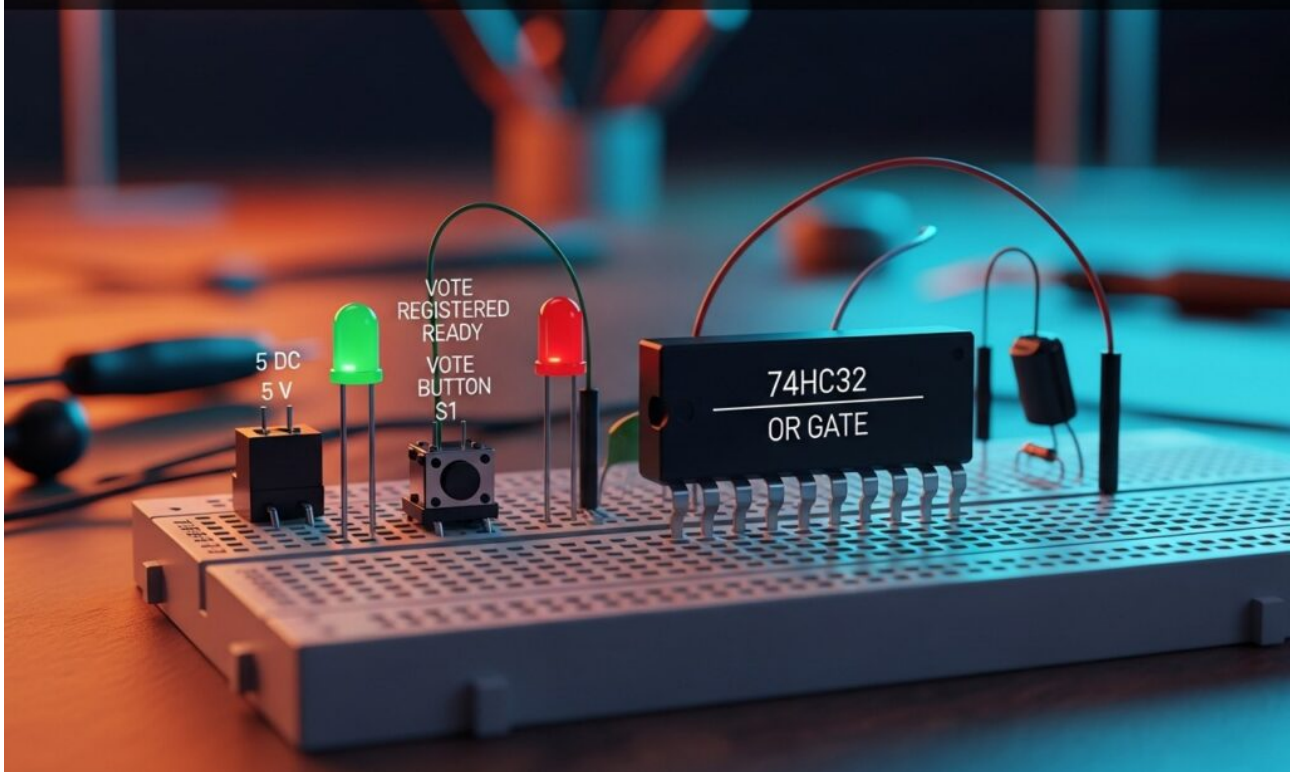

Master Digital Electronics by building a voting system with an OR gate. Design a circuit that triggers a visual signal when any judge activates a switch.