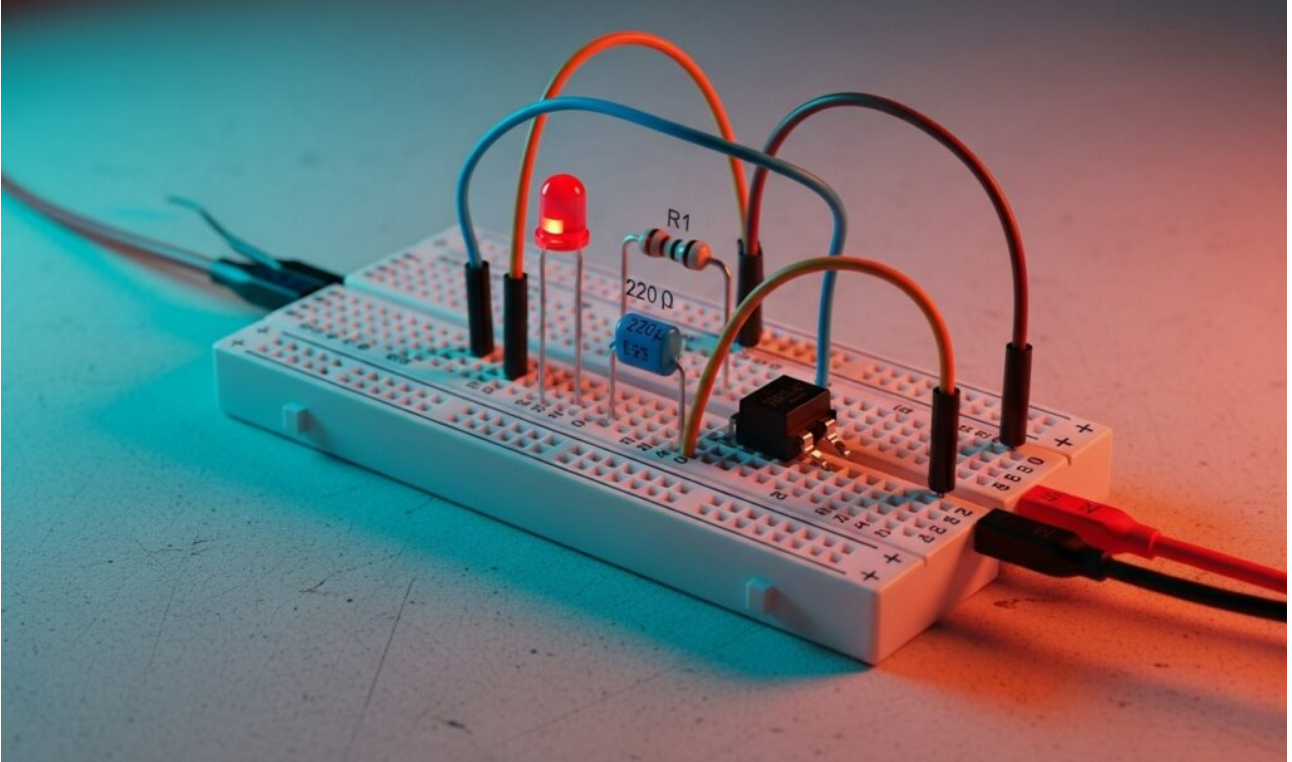


Practical case: Current limiting in an LED

Current limiting in an LED



Master Analog Electronics basics by building a circuit where a Resistor protects an LED. Apply Ohm's Law to limit current and ensure safe, steady illumination.