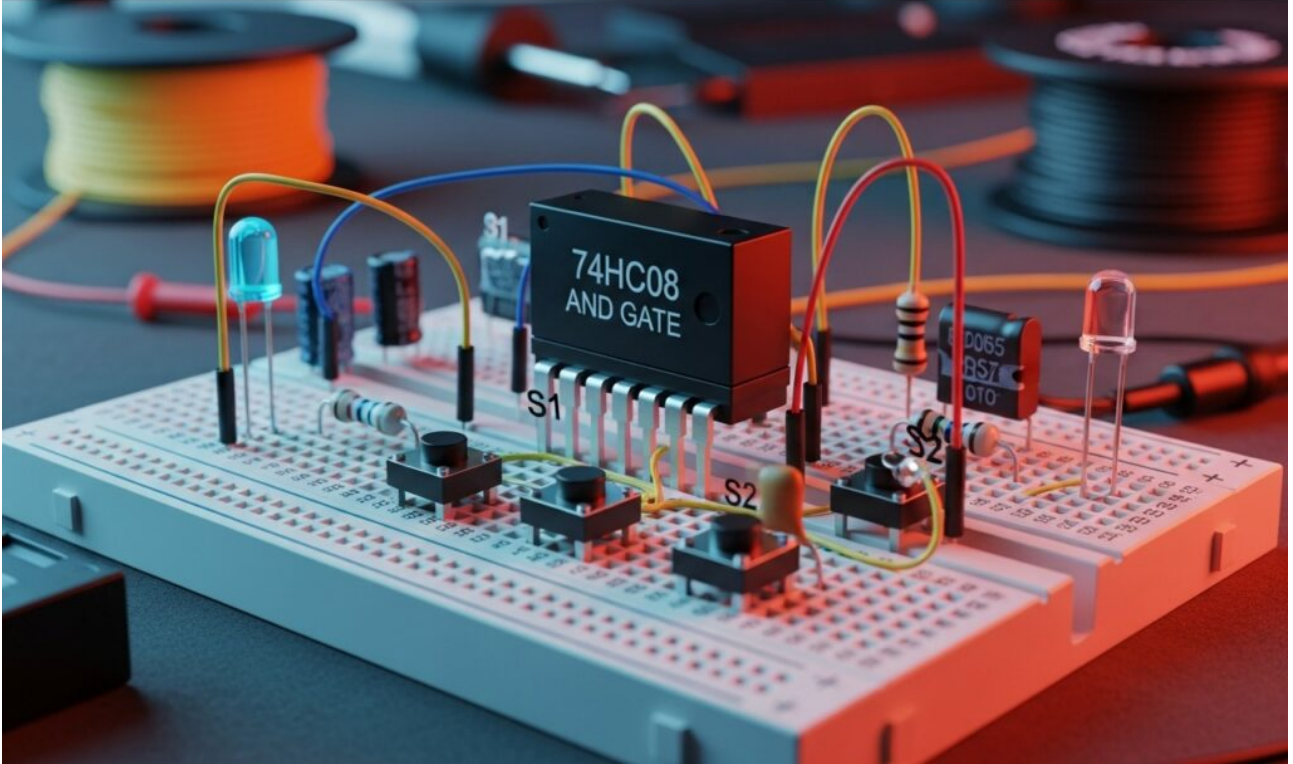


Practical case: Double Key Security System

Double Key Security System



Master Digital Electronics by building a dual-key security alarm with an AND gate. Learn to control logic signals and activate an LED only when inputs match.