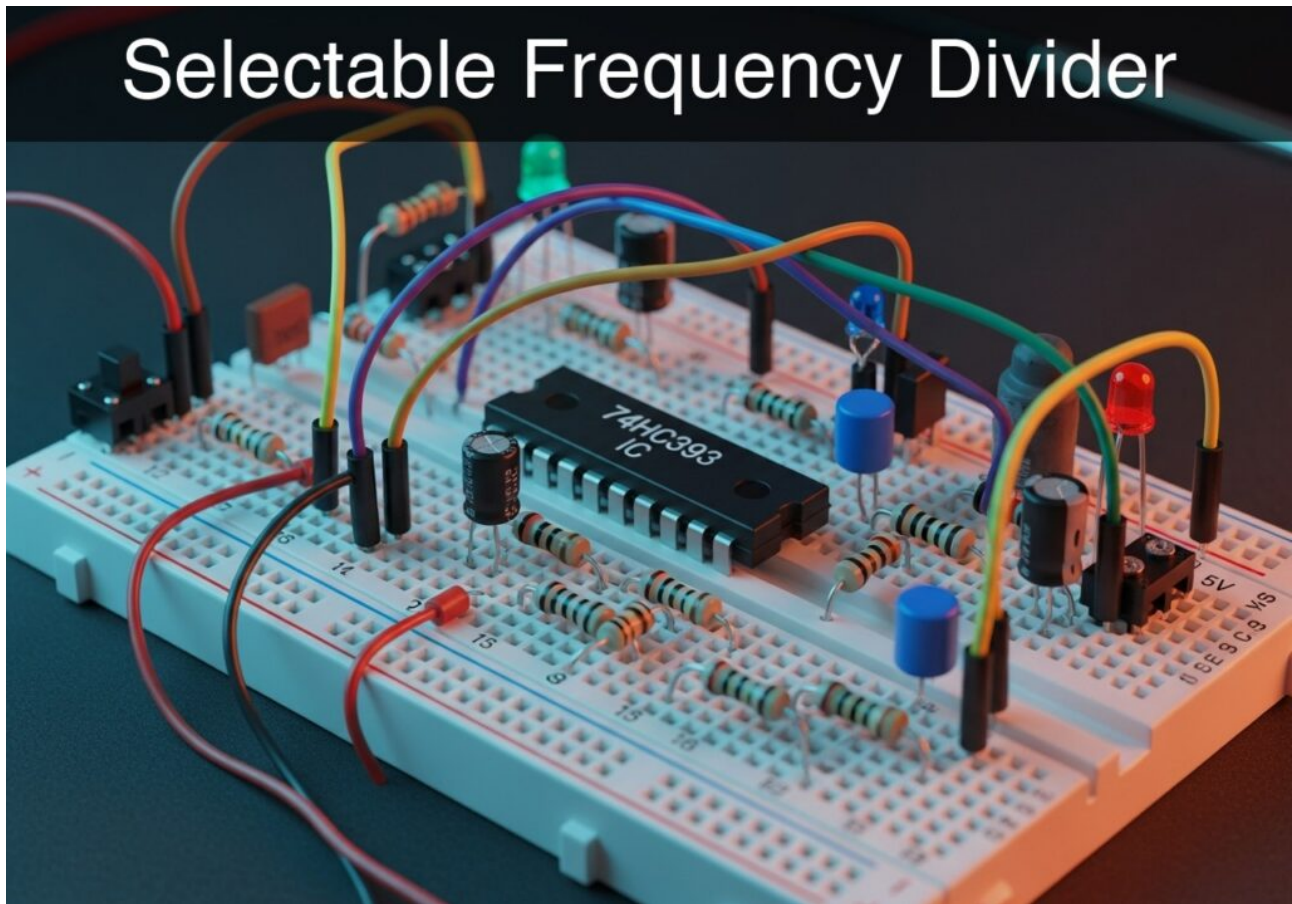


Practical case: Selectable Frequency Divider



Level: Medium - Build a binary frequency divider using a 74HC393 ripple counter with a selectable output stage.