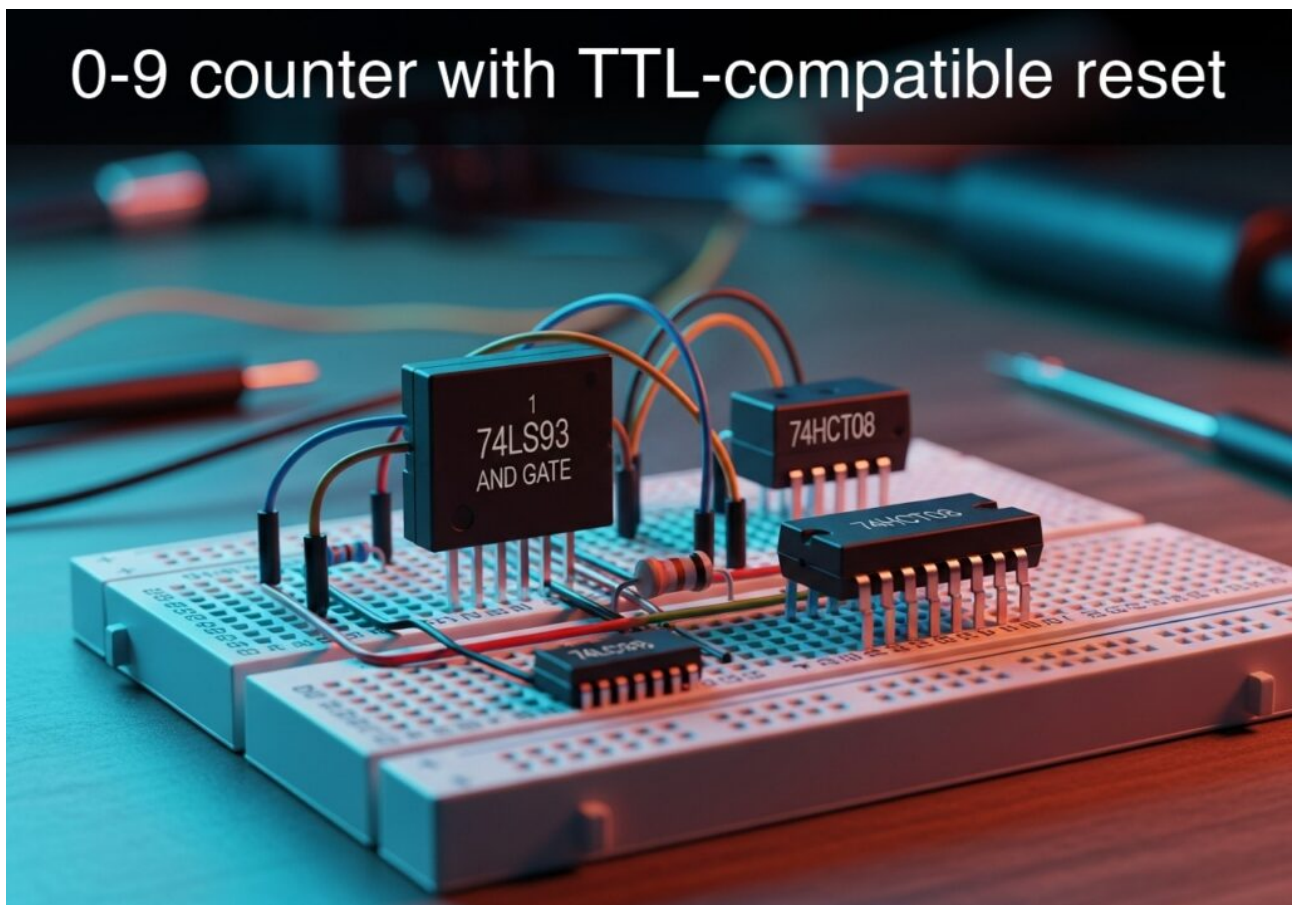


## Practical case: 0-9 counter with TTL-compatible reset



Level: Medium — Build a decimal counter that advances from 0 to 9 and resets automatically using a TTL-compatible AND gate.


## Objective and use case

You...

---

## Practical case: Conveyor belt object counter

# Conveyor belt object counter

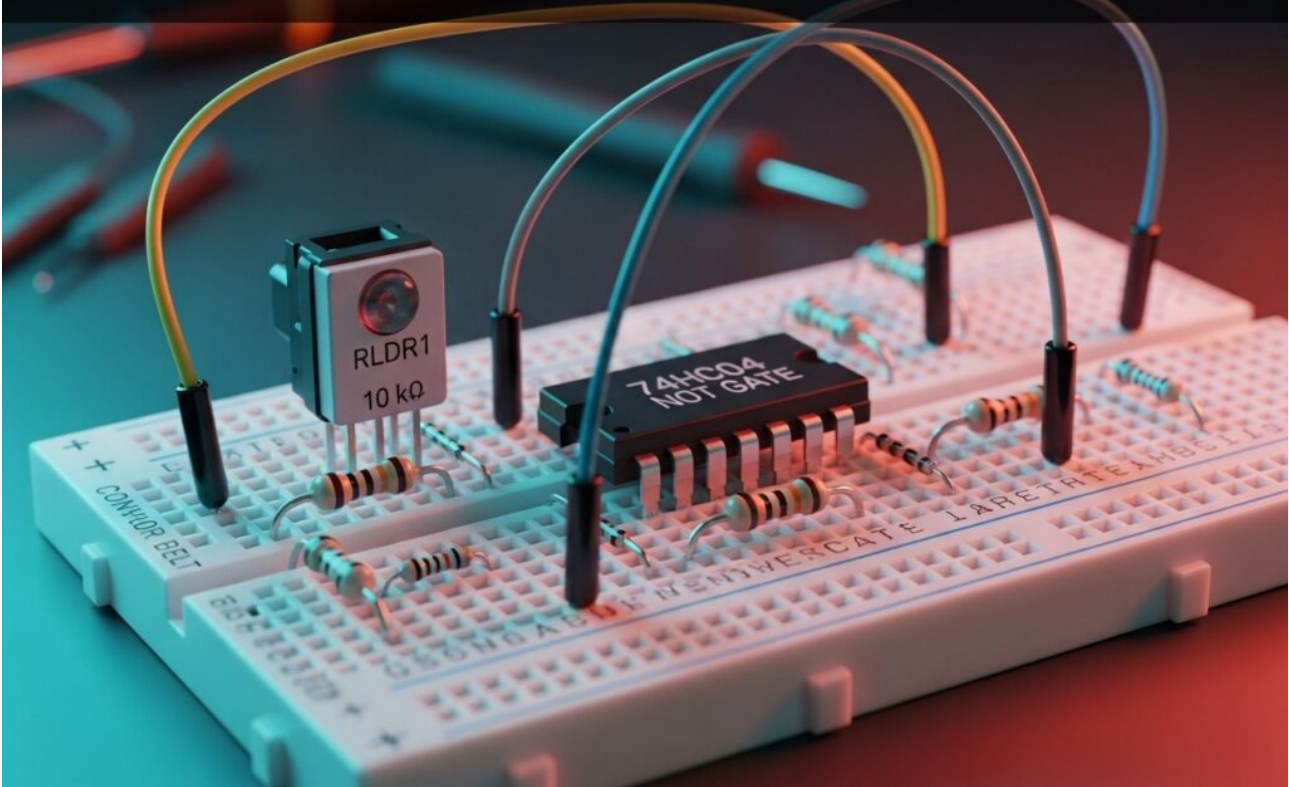

Level: Medium - Build an optical object counter with decimal outputs and an automatic batch reset.

## Objective and use case

In this practical case, you will...