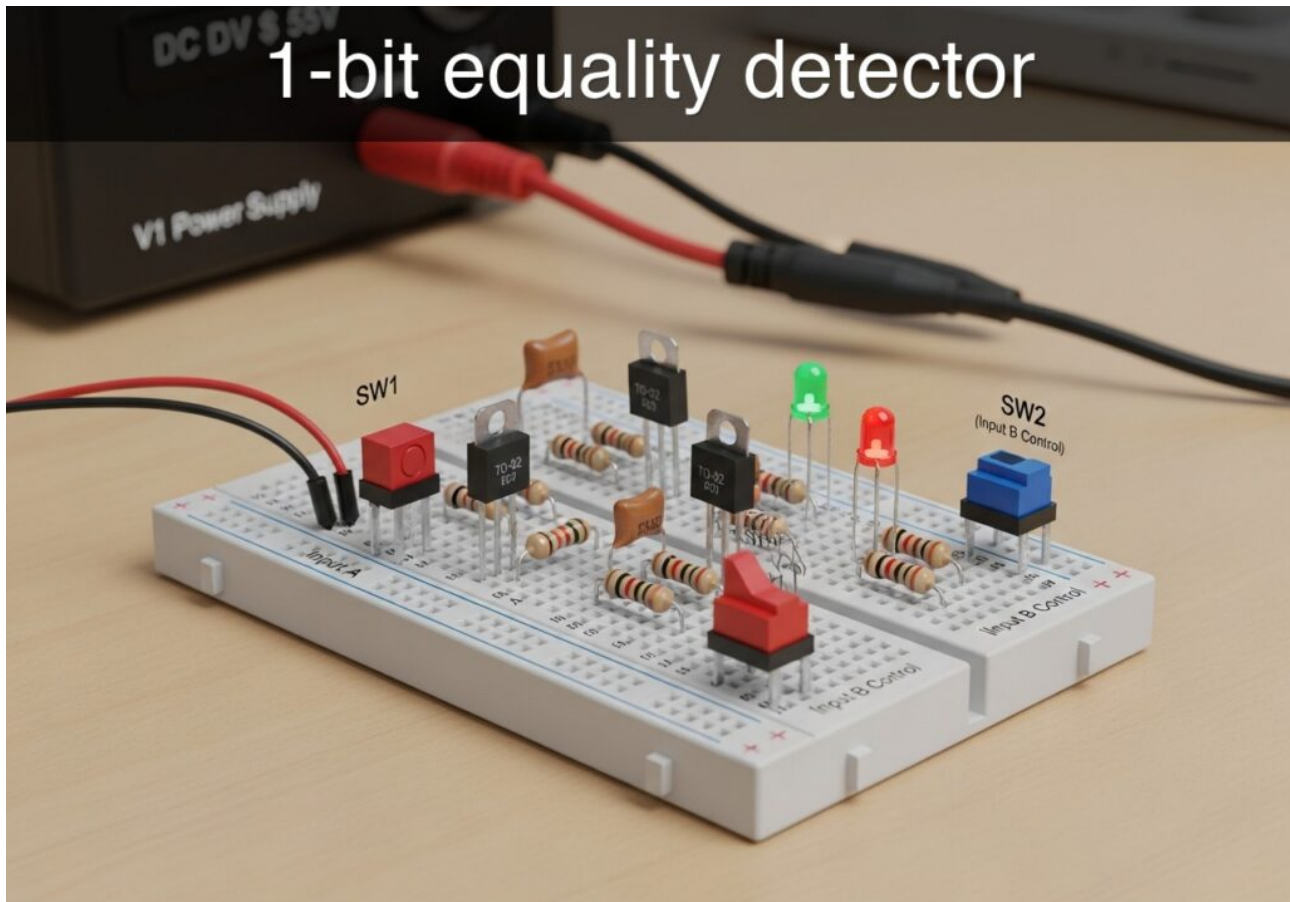


Practical case: 1-bit equality detector



Level: Basic - Verify the operation of a 74HC7266 XNOR gate as a logical equality detector using its truth table.