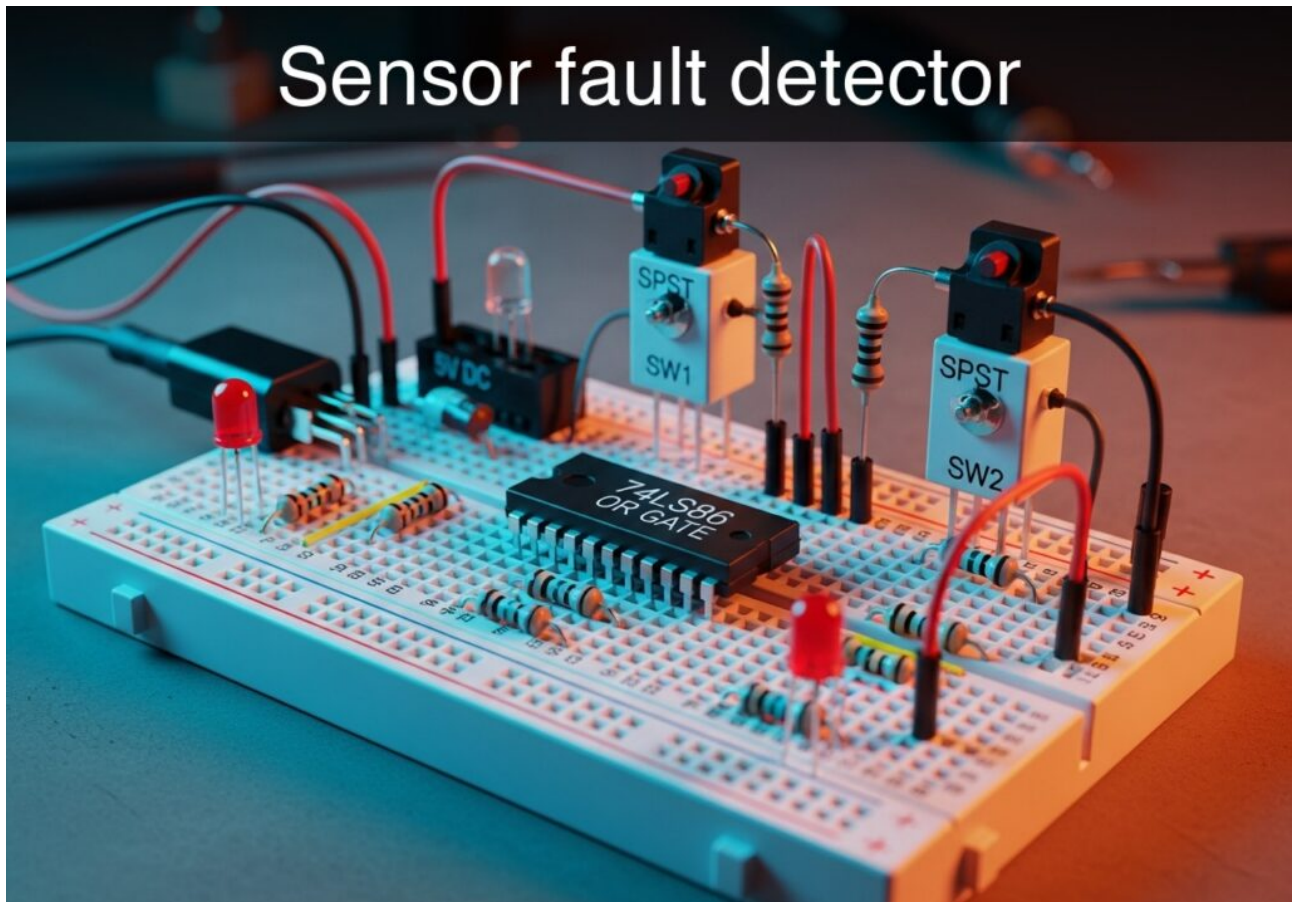


Practical case: Sensor fault detector



Level: Basic - Implement an XOR gate circuit to activate a visual alarm when two redundant sensors present different logic states.