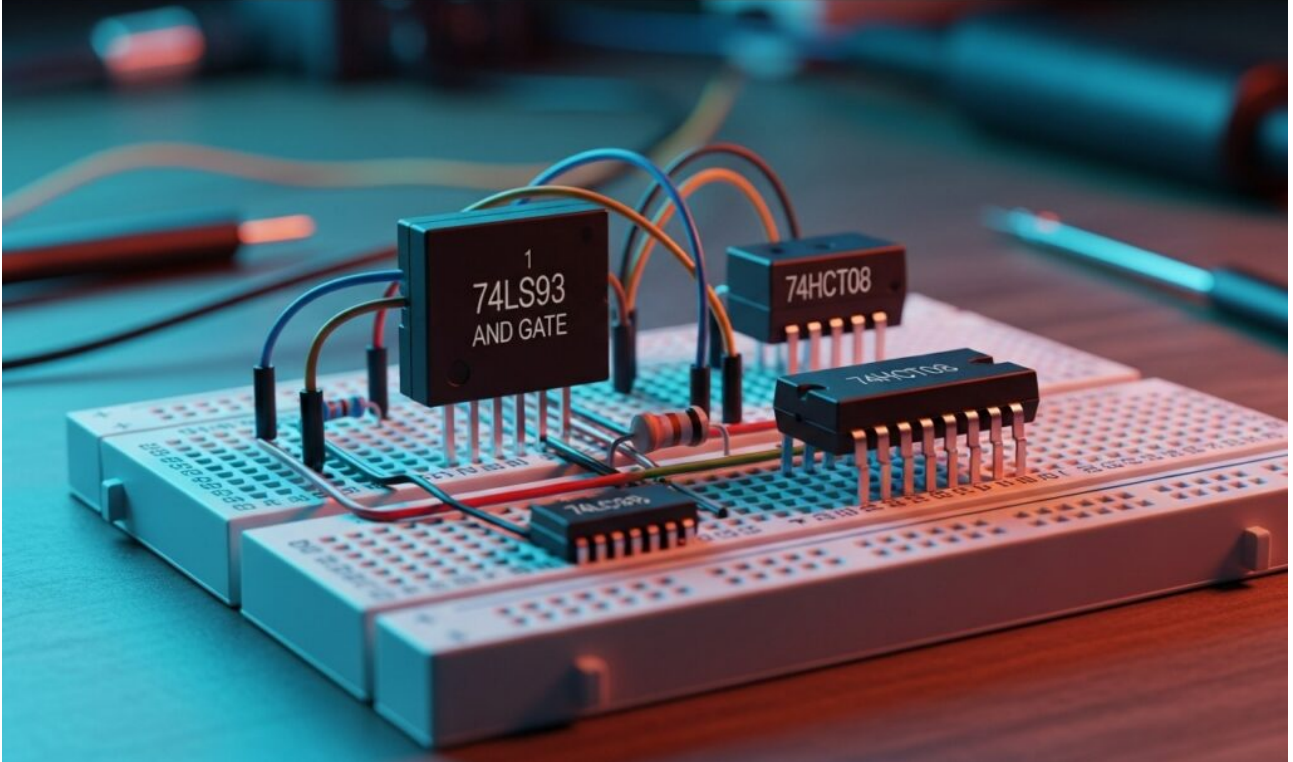


Practical case: 0-9 counter with TTL-compatible reset

0-9 counter with TTL-compatible reset



Level: Medium — Build a decimal counter that advances from 0 to 9 and resets automatically using a TTL-compatible AND gate.

Objective and use case

You...