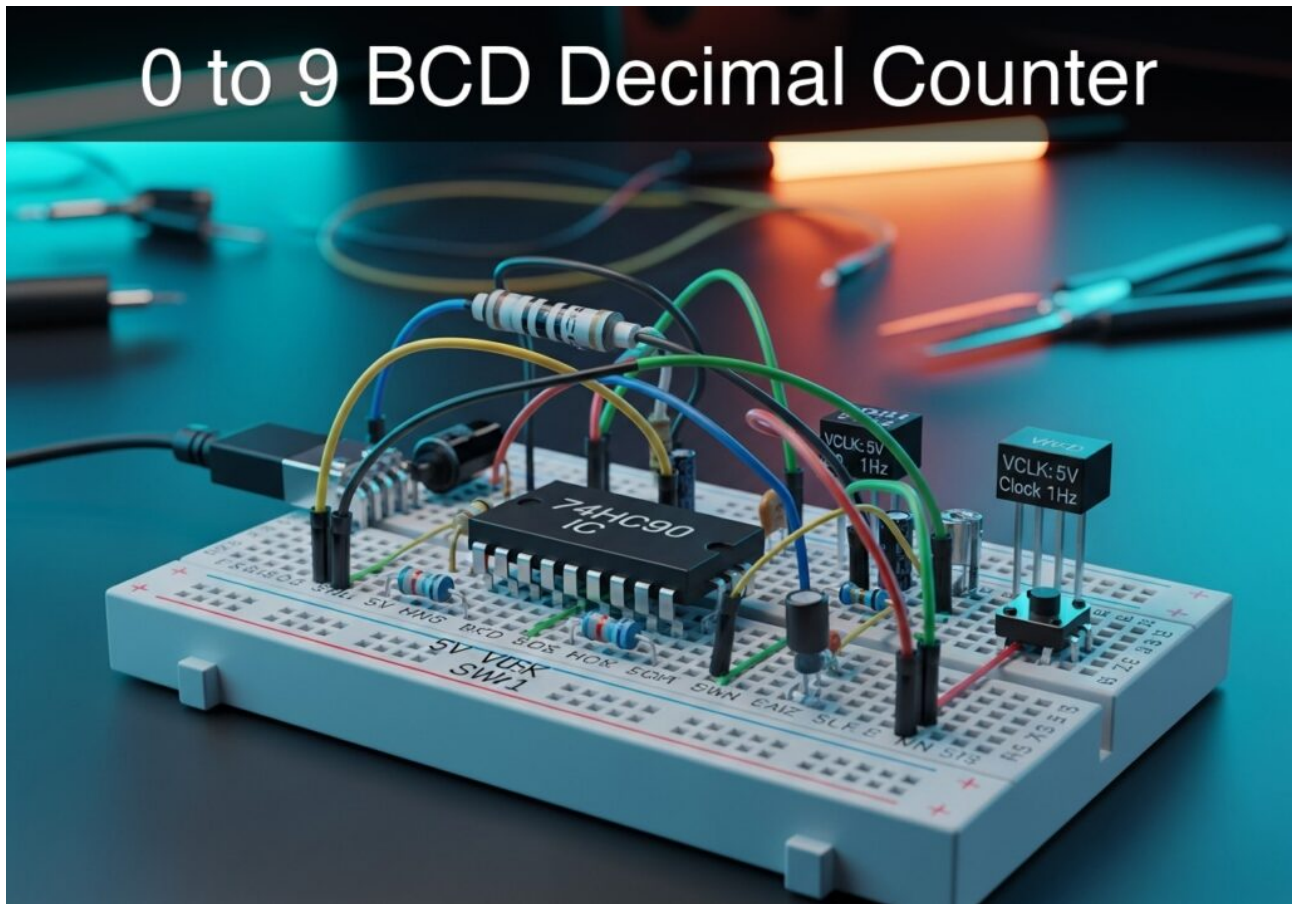


Practical case: 0 to 9 BCD Decimal Counter



Level: Medium | Build a 0-9 BCD counter using the 74HC90 IC to visualize binary progression via LEDs.