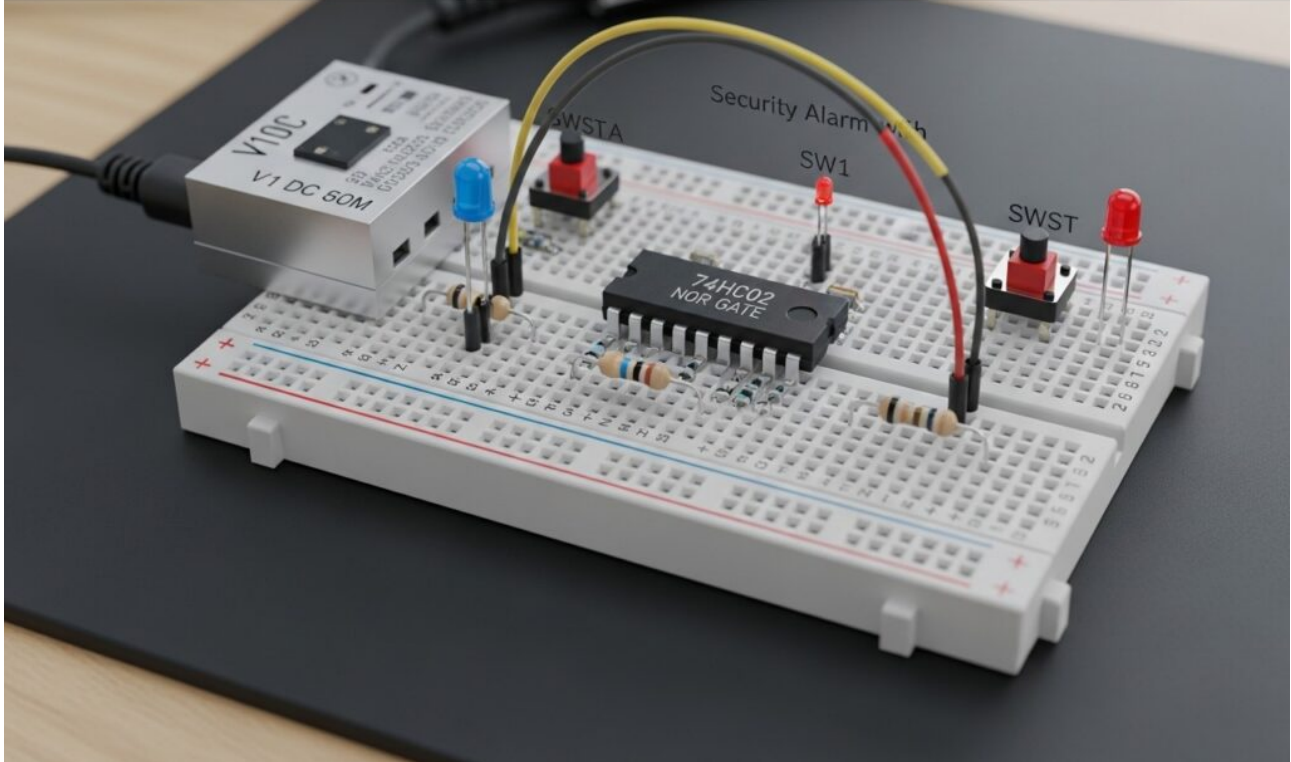


Practical case: Security alarm with NOR

Security alarm with NOR



Level: Basic | Objective: Verify the NOR gate truth table using an alarm circuit that activates only when no sensors detect movement.