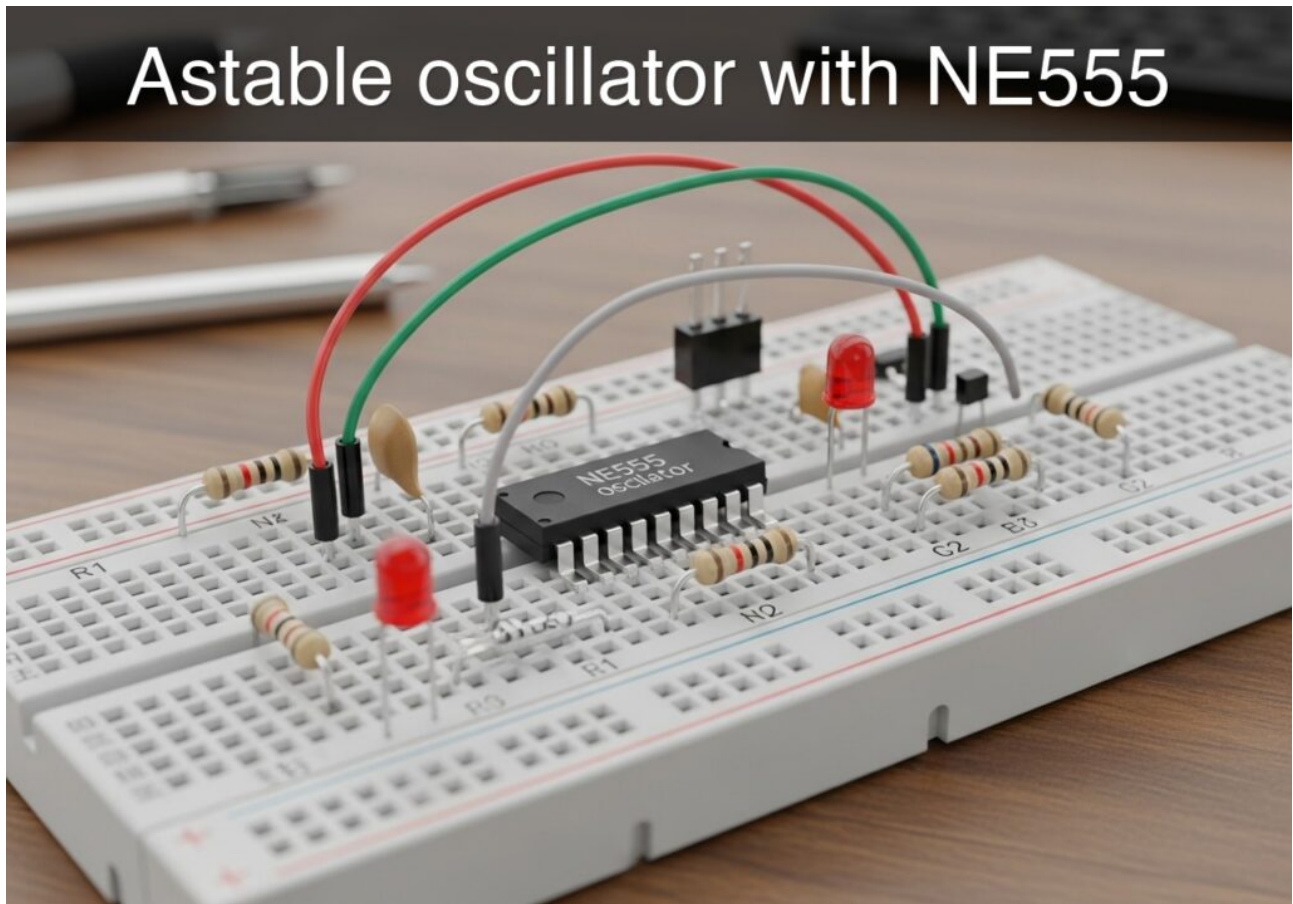


Practical case: astable oscillator with NE555



Level: Basic — Build an NE555 astable timer that blinks an LED at a visible frequency.

Objective and use case

You will build a simple astable timer with...

Practical case: One-Shot Timer Using NE555

