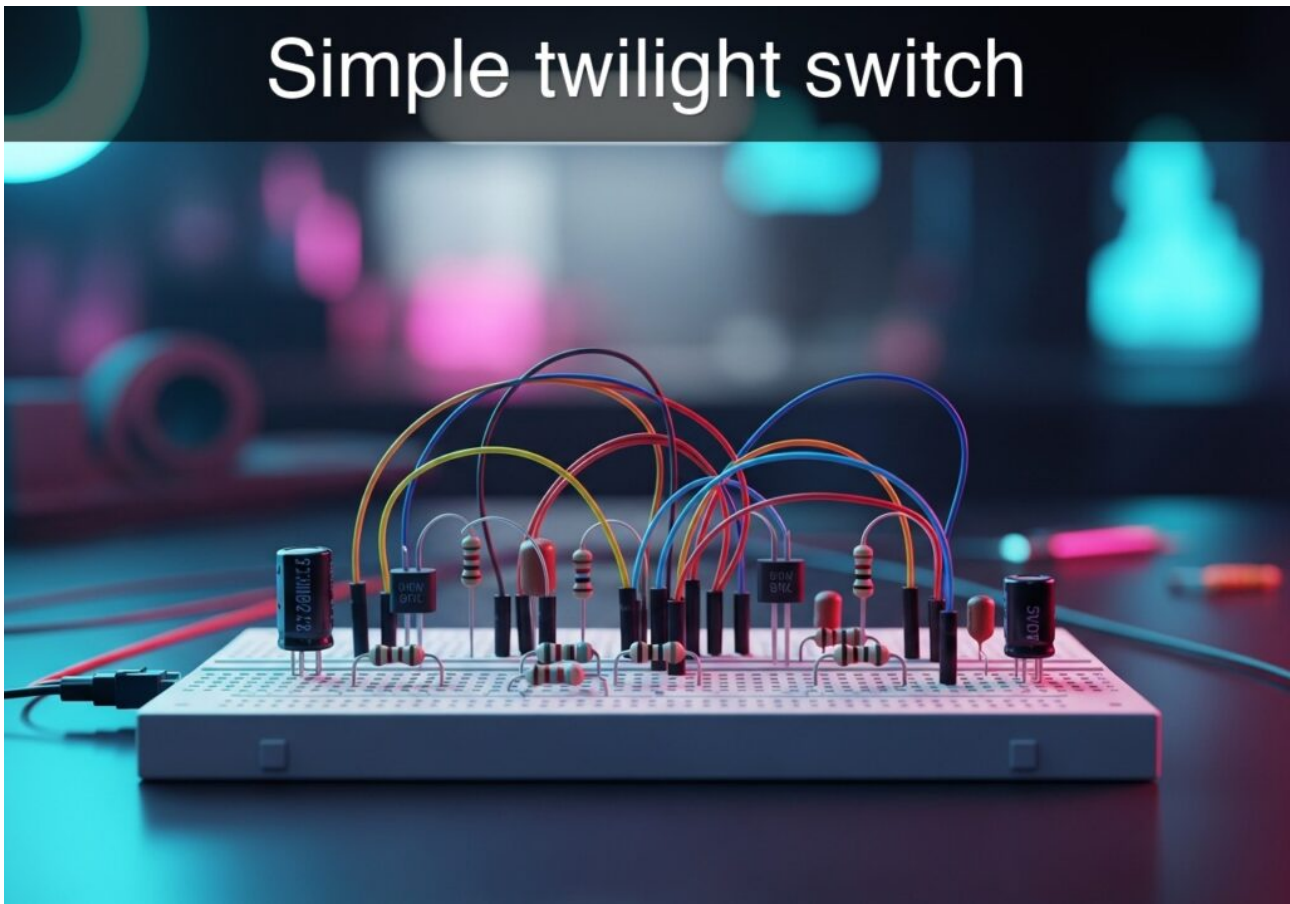


## Practical case: Simple twilight switch




Learn Analog Electronics by building a dark sensor circuit. Use a Photodiode to switch an LED on when light drops, mastering transistor switching logic.

---

## Practical case: Reverse Bias Photodiode Light Detection
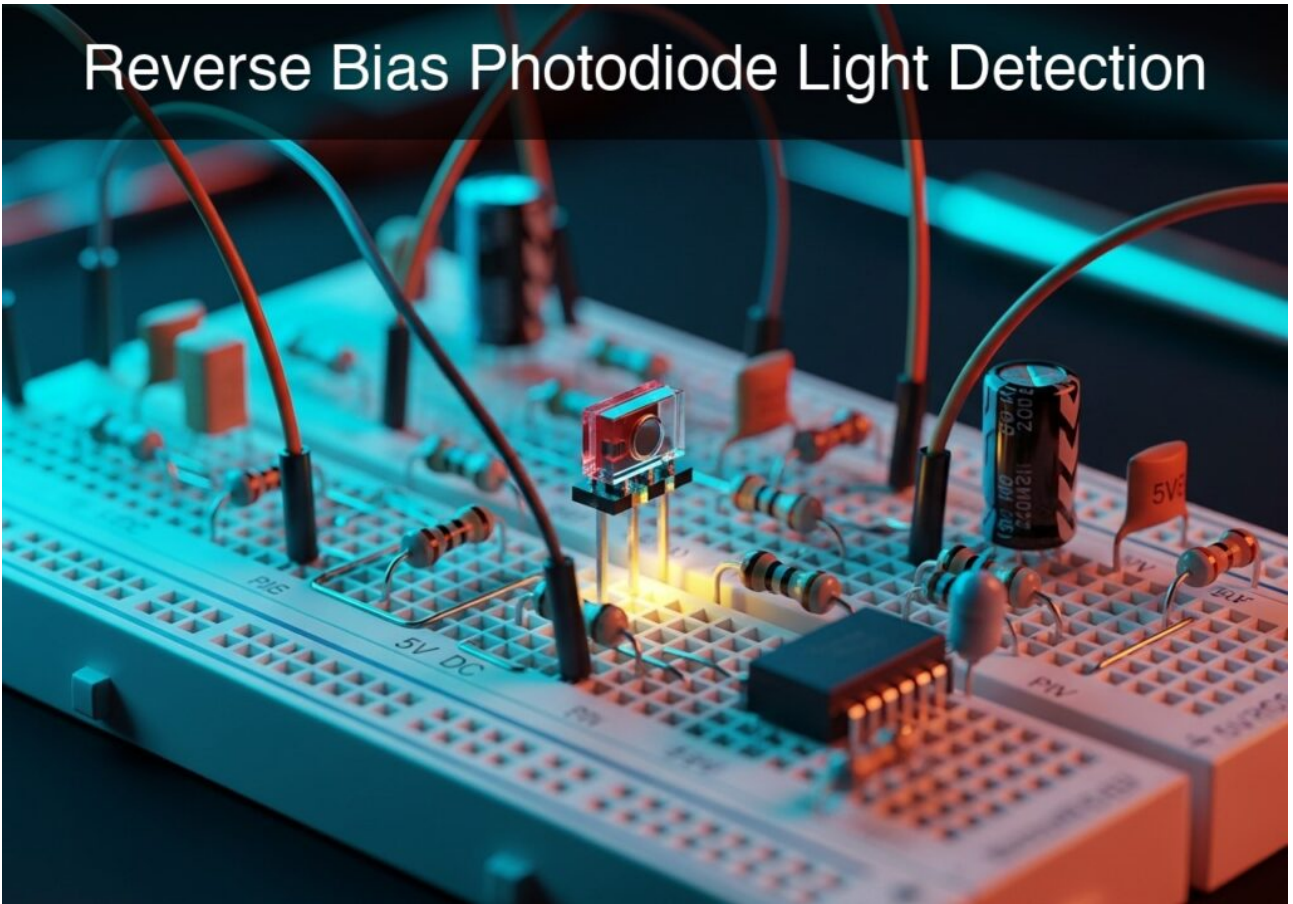
# Reverse Bias Photodiode Light Detection



Master Analog Electronics by building a light sensor circuit using a reverse-biased Photodiode. Measure linear voltage changes based on light intensity.