

## Practical case: Latching Alarm System




Master Analog Electronics by building a self-latching Relay circuit. Create a reliable alarm memory system that holds active states until manually reset.

---

## Practical case: DC motor control with relay and pushbutton
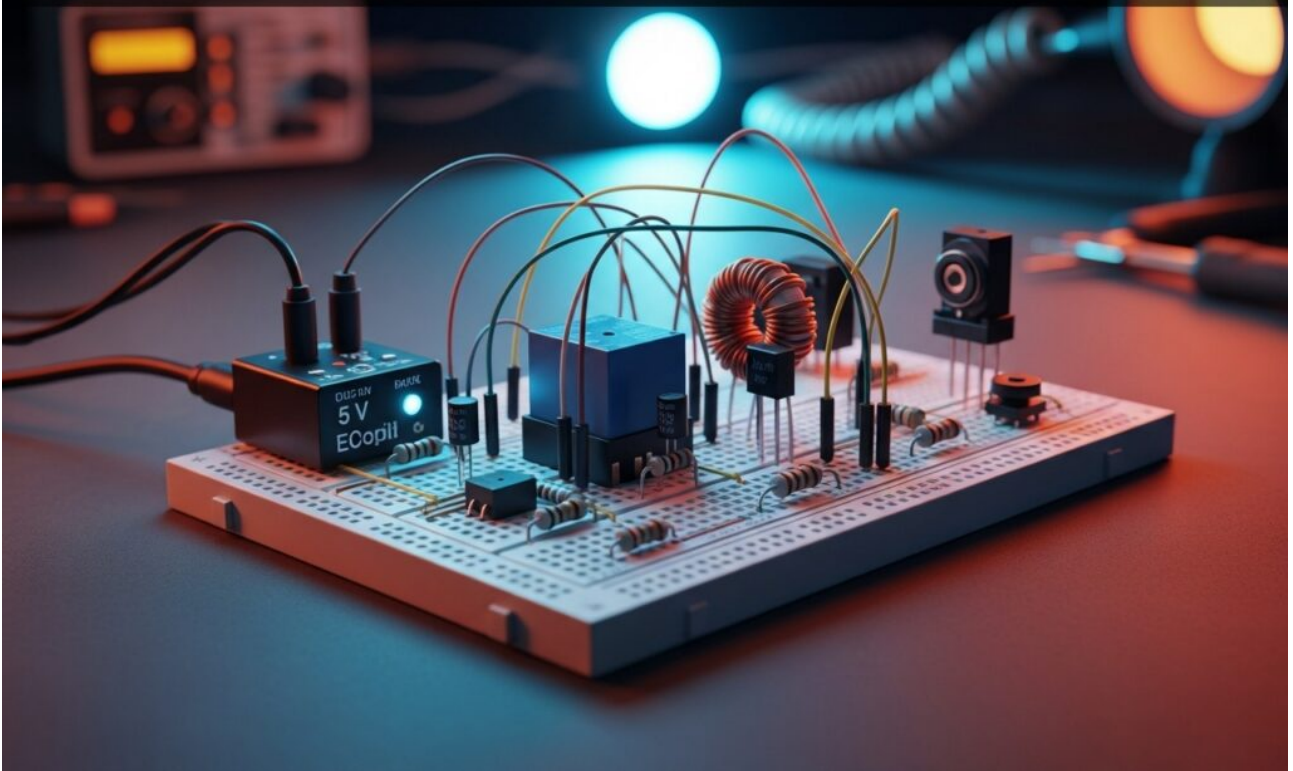
# DC motor control with relay and pushbutton



Master Analog Electronics by building a Relay circuit to safely control high-power motors. Learn to isolate signals and achieve reliable switching protection.