Practical case: One-Shot Timer Using NE555

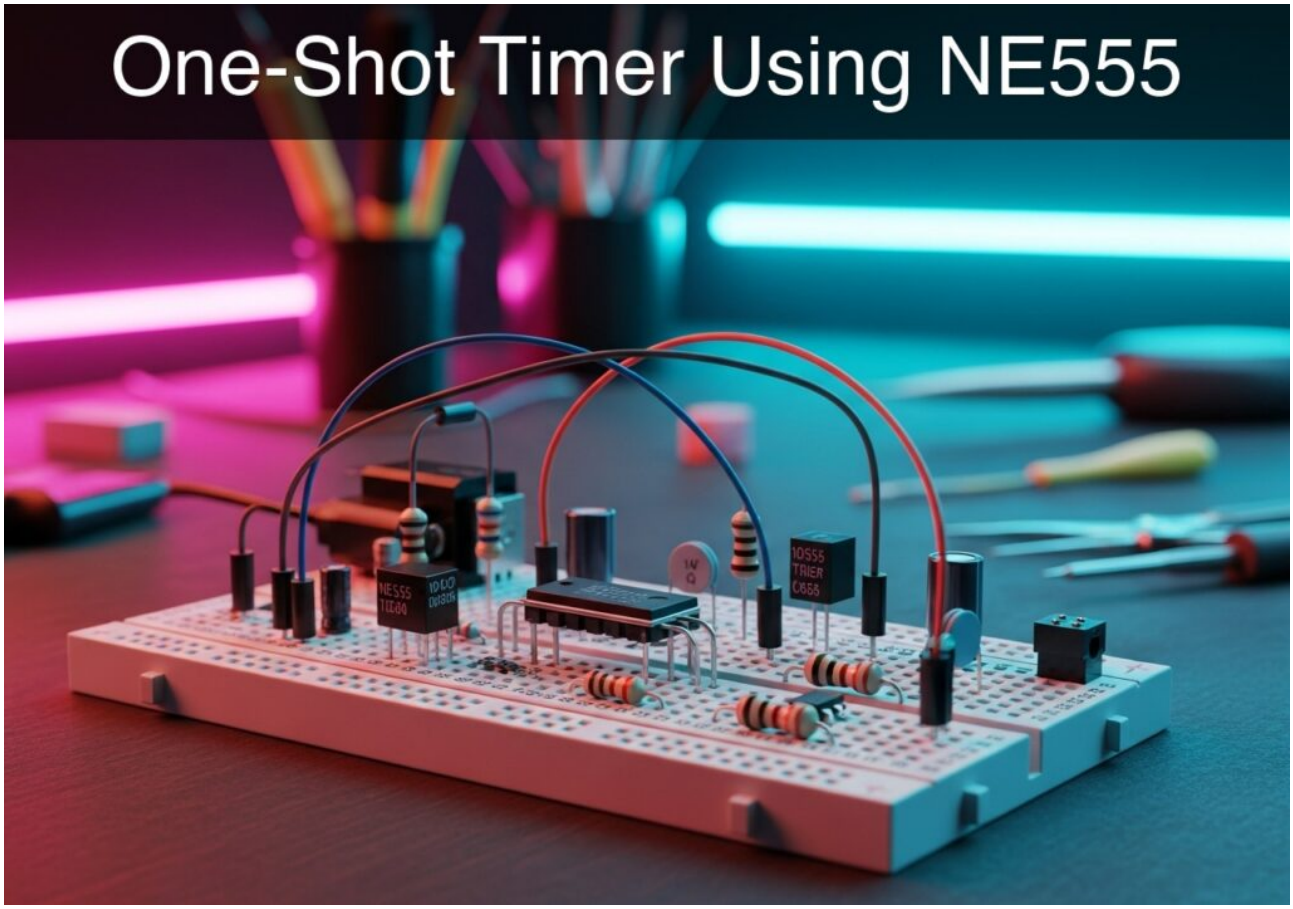

Level: Basic – Build a monostable timer circuit using the NE555 IC to control an LED output for a set duration.

Objective and use case
In this practical…